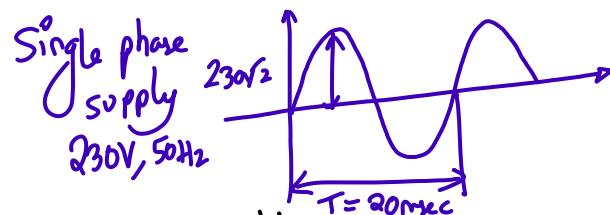


Module 2: AC Circuits



Unit 2.1: Generation of alternating voltage, average value, RMS value, form factor, phasor representation in rectangular and polar form, crest factor

- ① Alternating current: When the current in the circuit varies in magnitude as well as direction periodically \rightarrow it is called "alternating current"

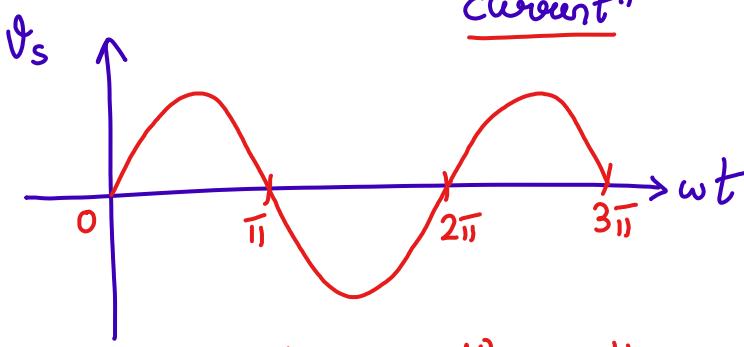


fig1: Sinusoidal alternating voltage

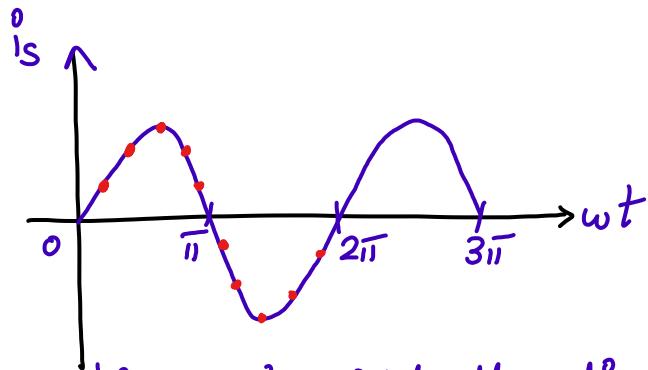


fig2: Sinusoidal alternating current

- ② The circuits in which alternating currents flow's are called "AC circuits"


- ③ Advantages of AC:

a) Voltages in AC system's can be raised or lowered with the help of transformer.

b) Used in AC motor — simpler — lesser maintenance

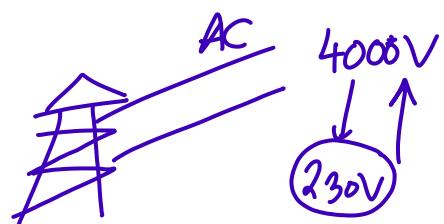c) AC can be easily converted to DC

Thus, AC is extensively used in practise (230-250V, 50Hz, 1φ)



Single phase

in residential areas.

* Generation of Alternating voltages:

- ① An alternating voltage can be generated either by
- a) by rotating a coil in a stationary magnetic field OR
 - b) by rotating a magnetic field within a stationary coil

- ② In both cases, the magnetic field is cut by the coils & an emf is induced in the coil.

Faraday's law
of electromagnetic
induction

- ③ Scheme for generation of AC voltage is shown in fig 3.

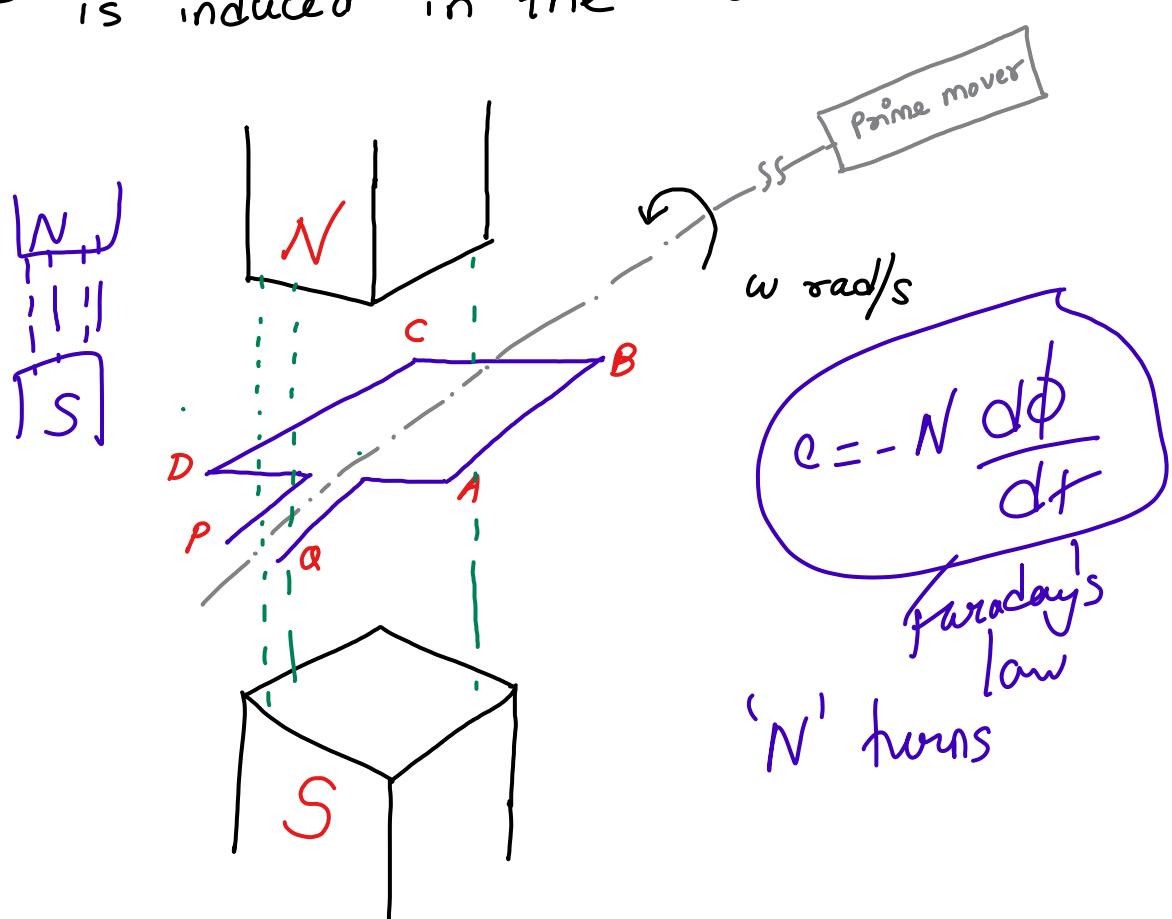


fig 3: Generation of alternating voltage

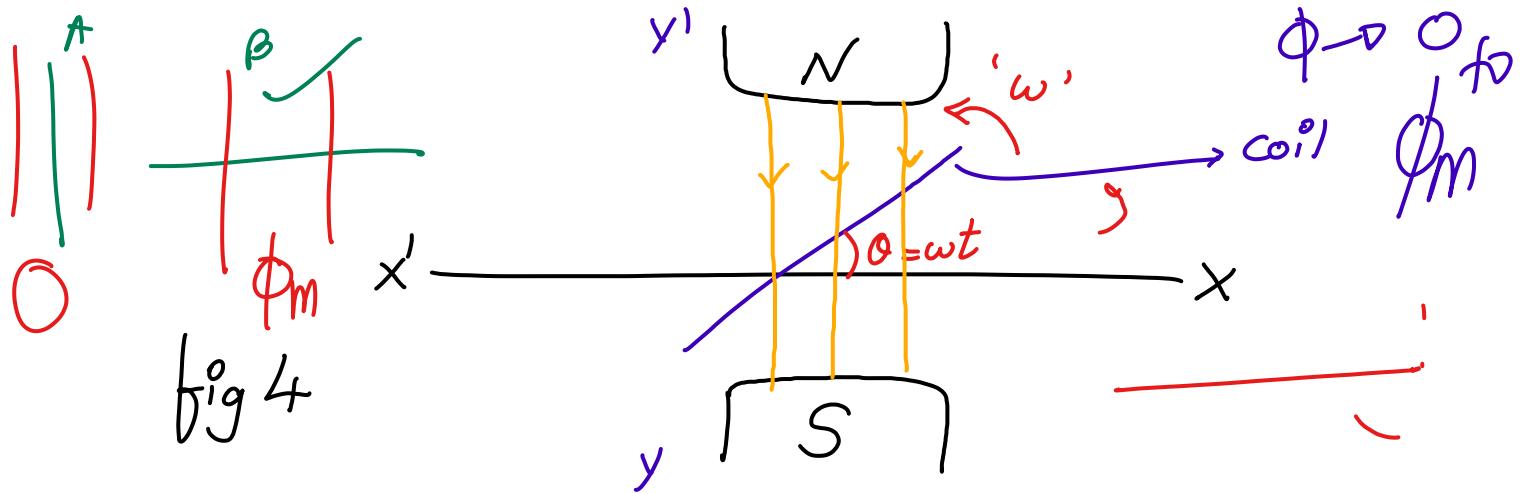


fig 4

- ④ Here, it consists of permanent magnet with two poles
- ⑤ A rectangular coil of N turns is rotating in anti-clockwise with angular velocity ω radians per seconds in a uniform magnetic field
- ⑥ When the coil cuts the magnetic line of flux \rightarrow an emf gets induced in it.
- ⑦ Let ϕ_m be the max flux cutting the coil when its axis coincides with XX' axis
- ⑧ When the coil is along YY' i.e parallel to lines of flux \rightarrow the flux linking with it is zero
- ⑨ Coil rotates through an angle $\theta = \omega t$ at any instant 't'
 - a) θ - angle between motion of the coil & direction of the magnetic field
- ⑩ The flux linkage of the coil is given by,

$$\omega t = \theta$$

$$\omega = 2\pi f = \frac{2\pi}{T}$$

$$\phi = \phi_m \cos \omega t = \phi_m \cos \theta \quad \text{--- (1)}$$

(11) As per Faraday's law of electromagnetic induction,

$$e = -N \frac{d\phi}{dt}$$


$$\phi = \phi_m \sin \omega t$$

$$\therefore e = -N \frac{d}{dt} (\phi_m \cos \omega t)$$

$$\therefore e = N \phi_m \omega \sin \omega t$$

$$\therefore e = E_m \sin \omega t \quad \text{--- (2)}$$

$$\omega t = 0$$

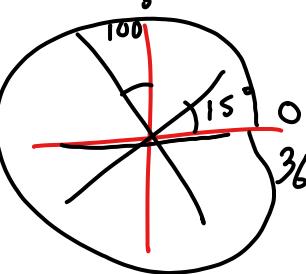

$$\text{where, } E_m = N \phi_m \omega$$

↳ maximum value of induced emf

$$e(\omega t) \quad e = E_m \sin \omega t$$

(12) 'e' is the instantaneous value of the induced emf (voltage) in a coil

$$e = E_m \sin \omega t$$

a) e depends on θ ($\theta = \omega t$)

b) As the coil continuously rotates with constant angular velocity 'w' (i.e. $\theta = \omega t$ varies from 0° to 360°) the magnitude of induced emf in a coil varies continuously.

$$e = E_m \sin \theta = E_m \sin \omega t$$

(13) $\theta = 0^\circ \rightarrow$ no emf $\rightarrow e = 0$

$\theta = 0$ to $360^\circ \rightarrow$ coil complete one rotation

14) Taking different instants ie position of the coil \rightarrow
 the induced emf in the coil is calculated as
 follows:-

$$e = E_m \sin \theta = E_m \sin \omega t$$

$$90 \times \frac{\pi}{180}$$

- i) $\theta = 0^\circ \rightarrow \sin 0^\circ \rightarrow e = 0V$
- ii) $\theta = 90^\circ \rightarrow (\omega t = \frac{\pi}{2}) \rightarrow \sin 90^\circ \rightarrow e = E_m \text{ Volts}$
- iii) $\theta = 180^\circ \rightarrow \sin(180^\circ) \rightarrow e = 0V$
 $(\omega t = \pi)$
- iv) $\theta = 270^\circ \rightarrow \sin(270^\circ) \rightarrow e = -E_m \text{ Volts}$
 $(\omega t = \frac{3\pi}{2})$
- v) $\theta = 360^\circ \rightarrow \sin(360^\circ) \rightarrow e = 0V$
 $(\omega t = 2\pi)$

$$e = E_m \sin \omega t$$

$$E_m \sin \theta$$

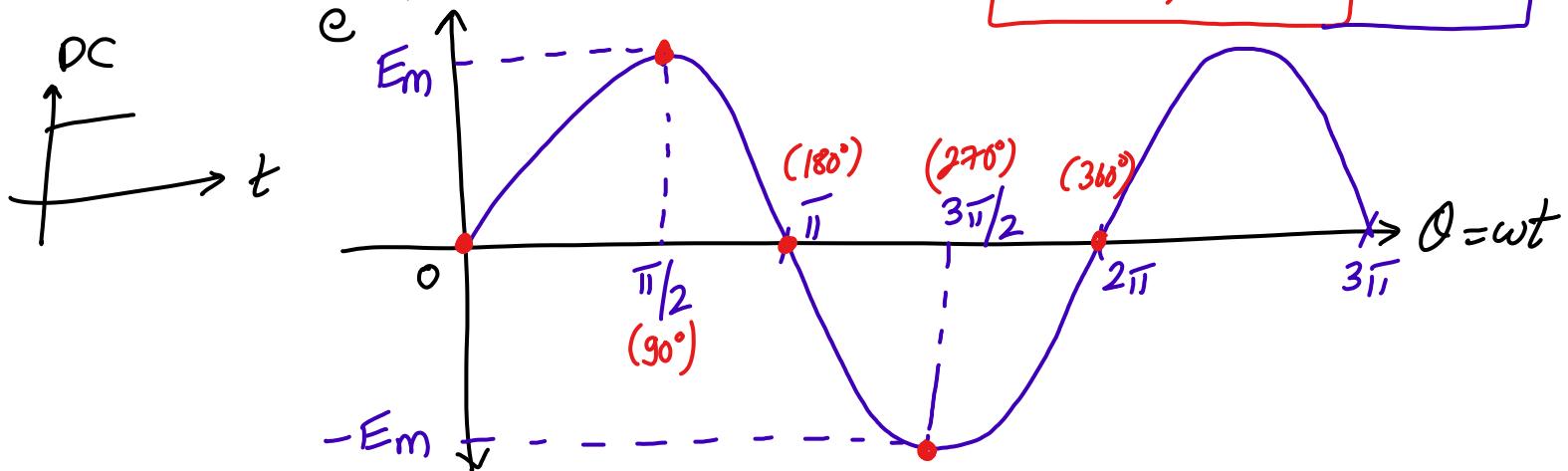


Fig 4: Generated sinusoidal alternating voltage


14) By plotting induced emf 'e' against the position of the coil (i.e. $\theta = \omega t$), we get sinusoidal alternating waveforms as shown in fig 4

15) Thus, the alternating voltage can be generated by rotating a coil with constant velocity w in a uniform magnetic field


* AC Terminology:

① Instantaneous value: The value of the alternating quantity at a particular instant of time is known as its instantaneous value.

eg $v_1(t)$ & $v_2(t)$

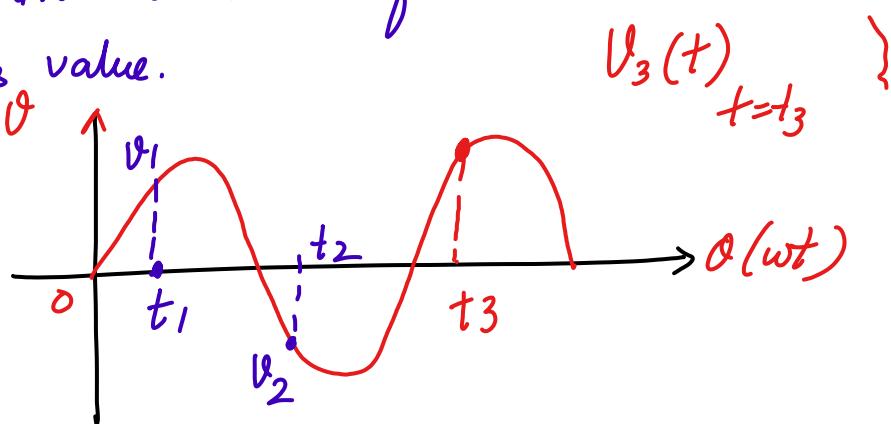

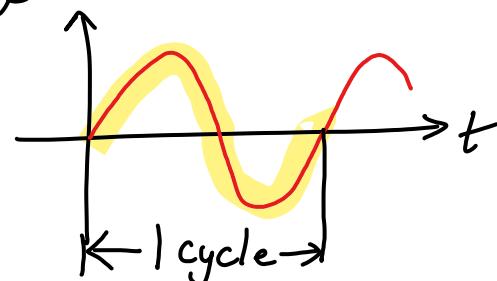
② Cycle: One complete set of positive and negative values of an alternating quantity is known as cycle



eg 1 cycle of sinusoidal AC voltage

③ Time period : (T): The time taken by an alternating quantity to complete one cycle is known as its time period.

time for
1 cycle (sec/cycle)

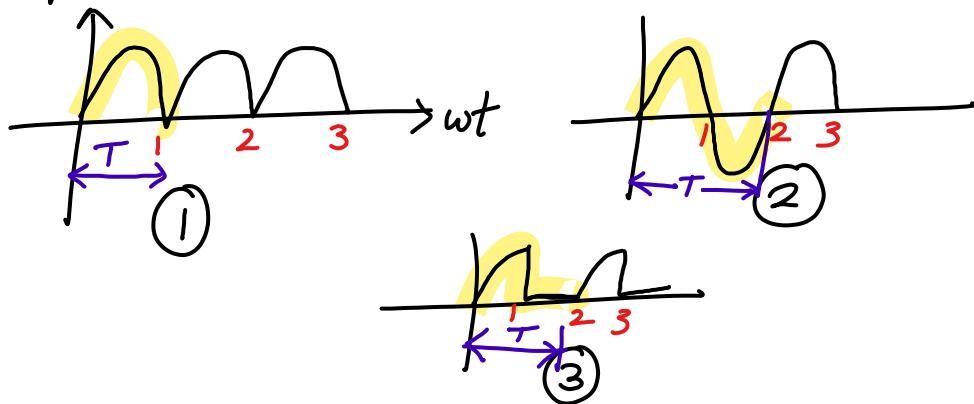

④ Frequency (f): The number of cycles completed by an alternating quantity per second is known as its frequency. It is denoted by 'f'

It is measured in cycles/seconds or hertz (Hz)

Frequency is reciprocal of the time period "50Hz"

$$f = \frac{1}{T} \text{ Hz}$$

\downarrow
 $T = 20\text{msec}$


⑤ Amplitude: The maximum +ve or -ve value of an alternating quantity

Peak-to-peak value of AC sig $\rightarrow 2Vm$

⑥ Phase: The phase of an alternating quantity is the time that has elapsed since the quantity has last passed through zero point of reference

⑦ Phase difference (ϕ):

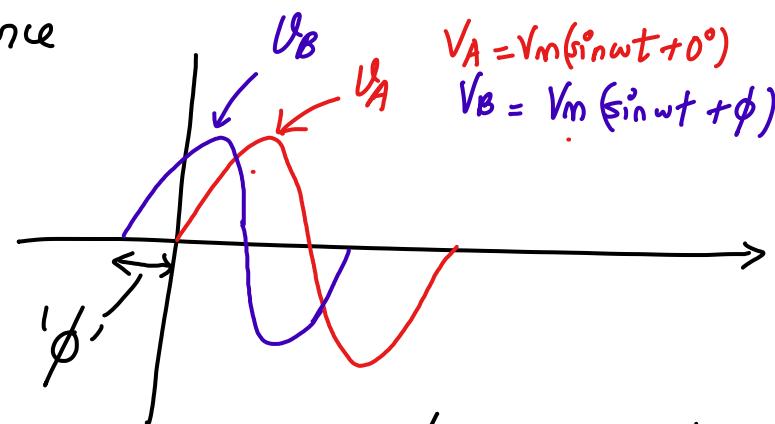Two alternating quantities are said to be in phase when they reach their maximum & zero values at the same time ϕ - phase angle



$$\left. \begin{aligned} V_A &= V_m \sin \omega t \\ V_B &= V_m \sin(\omega t + \phi) \end{aligned} \right\} \rightarrow V_B \text{ leads } V_A \text{ by phase angle } \phi$$

* Standard forms of Alternating quantities:

$$V = V_m \sin^o \theta$$


$$\theta = V_m \sin^o \omega t \quad (\theta = \omega t)$$

$$\theta = V_m \sin^o 2\pi f t \quad (\omega = 2\pi f)$$

$$\theta = V_m \sin^o \left(\frac{2\pi}{T} \right) t \quad (f = \frac{1}{T})$$

→ AC voltage

$$\omega = \frac{2\pi}{T}$$

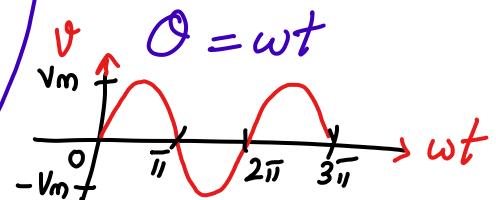


$$i = I_m \sin^o \theta$$

$$i = I_m \sin^o \omega t$$

$$i = I_m \sin^o (2\pi f t)$$

$$i = I_m \sin^o \left(\frac{2\pi}{T} \right) t$$

→ AC current

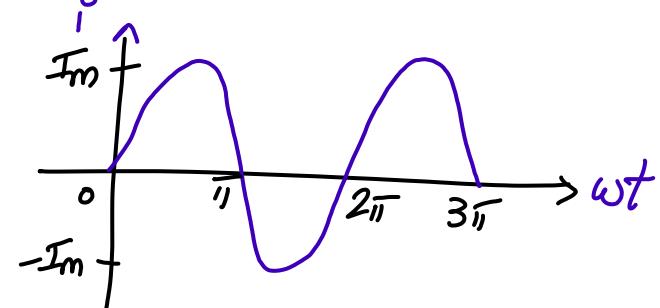

— x —

RL series circuit :

$V_R = IR$

$V_L = IX_L$

$V = IZ$

I

$\theta = \frac{V_{ms}}{V} \sin \omega t$


RL series circuit

- ① Consider a resistor 'R' & an inductor 'L' connected in series across an AC supply
- ② Let V = rms value of applied voltage
 I = rms value of circuit current
 Z = impedance of circuit

③ By ohm's law,

$V_R = IR$	$\rightarrow V_R$ is in phase with I
$V_L = IX_L$	$\rightarrow V_L$ leads I by 90°
$V = IZ$	


④ Phasor diagram

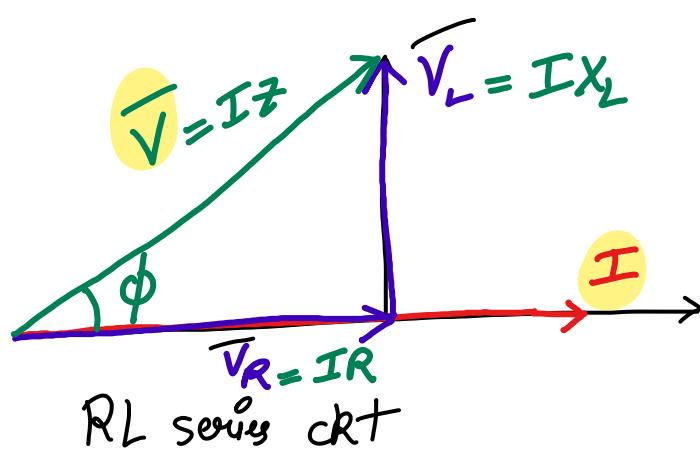

$$\sqrt{V} = \sqrt{V_L} + \sqrt{V_R}$$

$$\tan \phi = \frac{V_L}{V_R}$$

$$\cos \phi = \frac{V_R}{V}$$

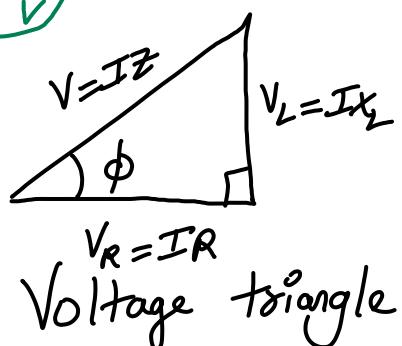

- a) ϕ is the phase angle of the circuit
- b) From phasor diagram \rightarrow Current 'I' lags behind the applied voltage 'V' by ϕ ($\phi < 90^\circ$)

c) Nature of the circuit is Inductive

$$\textcircled{5} \quad \tan \phi = \frac{V_L}{V_R} \rightarrow \phi = \tan^{-1} \left(\frac{V_L}{V_R} \right) = \tan^{-1} \left(\frac{I X_L}{I R} \right)$$

i.e. $\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$

\textcircled{6} Power factor (P.f) of the circuit

$$P.f = \cos \phi = \frac{V_R}{V} = \frac{I R}{I Z} = \frac{R}{Z}$$

P.f = $\frac{R}{Z}$ lagging


\textcircled{7} As the circuit current 'I' lags behind the applied voltage 'V' \rightarrow the nature of P.f is lagging

\textcircled{8} Impedance (Z): $Z^2 = R^2 + X_L^2$

a) Total opposition to the flow of AC current is Z

b) In voltage triangle \rightarrow
 \rightarrow Divide each voltage phasor by I

\downarrow
 we get Impedance triangle

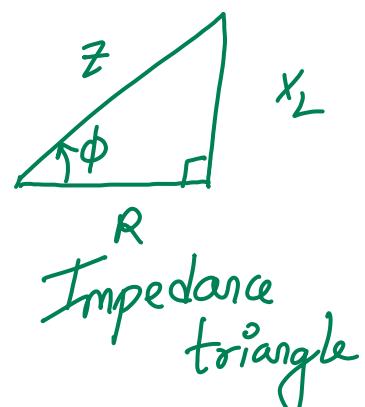

c) From impedance triangle,

$$Z = (R^2 + X_L^2)^{1/2}$$

d) Impedance Z can be expressed in rectangular & polar form $\bar{Z} = (R + j X_L) \underline{z}$ rectangular form

$$\bar{Z} = Z \angle \phi \rightarrow \dots \text{Polar form}$$

where,

$$Z = \sqrt{R^2 + X_L^2}; \quad \phi = \tan^{-1}\left(\frac{X_L}{R}\right)$$

(g) Power (P) :

a) Power that is actually consumed in the circuit is called

"Active or True" Power (in case of R)

b) Circulating power is called "Reactive power" (in case of L & C)

c) In case of resistance \rightarrow current 'I' is in phase with voltage 'V'

d) In case of inductance & capacitive
 \hookrightarrow Current 'I' is 90° out of phase with voltage

e) Active power 'P' = $V \times I$ (in phase with voltage)


Reactive power 'Q' = $V \times I$ (90° out of phase with voltage)

f) Circulating \rightarrow A pure inductor or a capacitor consume no power because all power received from AC source in a half cycle is returned to the source in the next half cycle \rightarrow This is circulating power

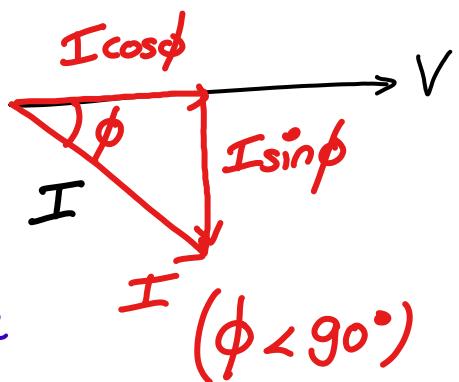g) Apparent power (S): It is the product of voltage & current in AC circuit

⑩ Taking V as reference phasor


\rightarrow Circuit current ' I ' can be resolved into two components
 1) $I \cos\phi$ is in phase with voltage
 2) $I \sin\phi$ is 90° out of phase with voltage



Phasor diagram figure 1,

⑪ In figure 1, if we multiply each of current phasor by V , we get the power triangle

$$S^2 = P^2 + Q^2$$

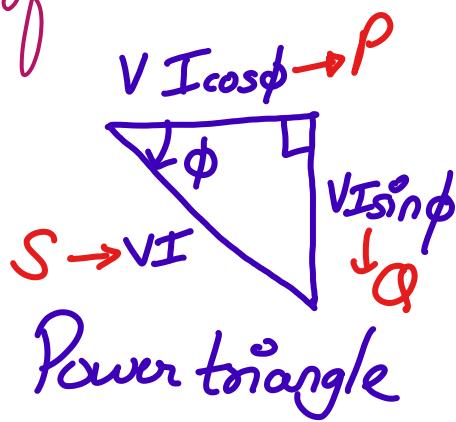

Power triangle

(12) Active power, $P = VI \cos \phi$ unit is W or KW
 Reactive power, $Q = VI \sin \phi$ unit is VAR or KVAR
 Apparent power, $S = VI$ unit is VA or KVA


$\cos \phi = \frac{P}{S}$

$P = I^2 R$
 $Q = I^2 X_L$
 $S = I^2 Z$

(volt-ampere-reactive)
↓
(volt-ampere)

Numerical 1: A coil has a resistance of 7Ω & an inductance of 31.8mH is connected to a $230V, 50\text{Hz}$ supply.

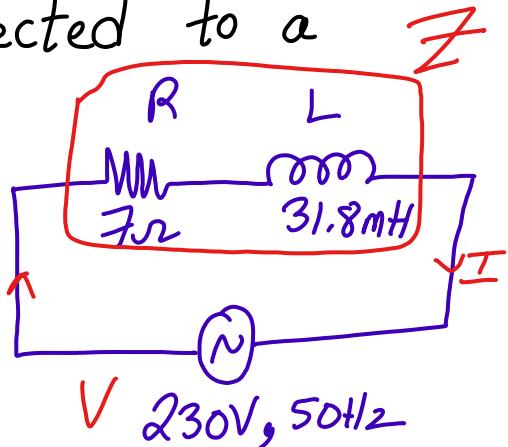Calculate : i) Circuit current (I)
 ii) Phase angle (ϕ)
 iii) Power factor (P.f)
 iv) Power consumed (P)



Solution: ① X_L ② Z ③ $I = \frac{V}{Z}$ ④ ϕ
 ⑤ $\text{P.f} = \cos \phi$ ⑥ $P = VI \cos \phi = I^2 R$

① $X_L = 2\pi f L = 2\pi \times 50 \times 31.8 \times 10^{-3} = 10\Omega$

② $Z^2 = R^2 + X_L^2 = 7^2 + 10^2 = 149 \rightarrow Z = \sqrt{149}$

$Z = 12.21\Omega$

$$\textcircled{3} \quad I = \frac{V}{Z} = \frac{230}{12.21} = 18.84A$$

$$\textcircled{4} \quad \text{Phase angle } \phi = \tan^{-1}\left(\frac{X_L}{R}\right) = \tan^{-1}\left(\frac{10}{7}\right)$$

$\phi = 55^\circ$

$$\textcircled{5} \quad \text{P.f} = \cos\phi = \cos 55^\circ = 0.574 \text{ lagging}$$

$$\textcircled{6} \quad P = VI \cos\phi = 230 \times 18.84 \times 0.574 = 2487 W$$

$$P = I^2 R = I^2 R = 18.84^2 \times 7 = 2487 W$$

OR (Different method):

$$\textcircled{1} \quad \bar{V} = 230 \angle 0^\circ V$$

$$\textcircled{2} \quad \bar{Z} = R + j X_L = 7 + 10j \Omega$$

$$\textcircled{3} \quad \bar{Z} = 12.20 \angle 55^\circ \Omega \quad (\bar{Z} = Z \angle \phi)$$

Shift Polar

$$\textcircled{4} \quad \phi = 55^\circ$$

$$\textcircled{5} \quad \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{230 \angle 0^\circ}{12.20 \angle 55^\circ} = 18.85 \angle -55^\circ A$$

$$\textcircled{6} \quad \text{P.f} = \cos\phi = \cos(55^\circ) = 0.574 \text{ lagging}$$

$$\textcircled{7} \quad P = VI \cos\phi = 2487W$$

↓
Numerical below

Numerical 2: Find γ and L


$$\textcircled{1} \quad I = \frac{V_R}{R}$$

$$\textcircled{2} \quad Z_{\text{coil}} = \frac{V_{\text{coil}}}{I}$$

$$\textcircled{3} \quad Z_{\text{coil}}^2 = \gamma^2 + X_L^2$$

$$\textcircled{4} \quad Z^2 = (R+r)^2 + X_L^2$$
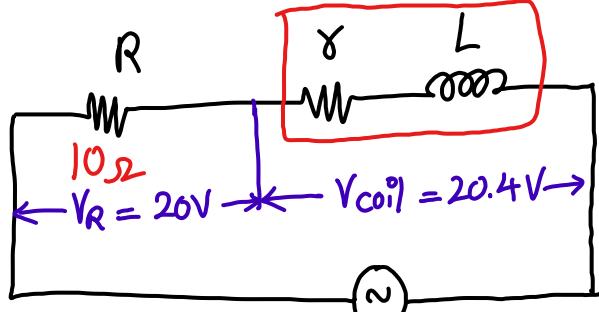
$$\textcircled{3} \text{ & } \textcircled{4} \quad \gamma \rightarrow L \quad ; \quad \textcircled{5} \quad Z = \frac{V}{I}$$



$$V_{\text{coil}} = I Z_{\text{coil}}$$

$$V_R = I R$$

$$\text{Solution: } \textcircled{1} \quad V_R = I R \rightarrow I = \frac{V_R}{R} = \frac{20}{10} = 2 \text{ A}$$

$$\textcircled{2} \quad V_{\text{coil}} = I Z_{\text{coil}} \rightarrow Z_{\text{coil}} = \frac{V_{\text{coil}}}{I} = \frac{20.4}{2} = 10.2 \Omega$$

$$\textcircled{3} \quad Z_{\text{coil}}^2 = \gamma^2 + X_L^2 = 10.2^2$$

$$\text{i.e. } \gamma^2 + X_L^2 = 10.2^2 - \textcircled{1}$$

$$\textcircled{4} \quad V = I Z \rightarrow Z = \frac{V}{I} = \frac{36}{2} = 18 \Omega$$

$$\textcircled{5} \quad Z^2 = (R+r)^2 + X_L^2$$

$$18^2 = (10+r)^2 + X_L^2 - \textcircled{2}$$

$$\textcircled{6} \quad \text{Eqn } \textcircled{2} - \text{Eqn } \textcircled{1} \rightarrow (10+r)^2 + X_L^2 - r^2 - X_L^2 = 18^2 - 10.2^2$$

$$\text{i.e. } 100 + 20r + r^2 - r^2 = 219.96$$

$$20r = 119.96$$

$$\boxed{\gamma \approx 6 \Omega}$$

$$\textcircled{7} \quad \text{From eqn } \textcircled{1}, \quad \gamma^2 + X_L^2 = 10.2^2$$

$$\text{i.e. } 6^2 + X_L^2 = 10.2^2$$

$$X_L^2 = 10.2^2 - 6^2 = 68.04$$

$$\boxed{X_L = 8.25 \Omega}$$

$$\textcircled{8} \quad X_L = 2\pi f L \rightarrow L = \frac{X_L}{2\pi f} = \frac{8.25}{2\pi \times 50}$$

$$\boxed{L = 0.022 \text{ H}}$$

—x—

Numerical 3: A current of 5A flows through pure resistance and a coil supplied at 250V, 50Hz
"H.W" If the voltage across the resistance is 125V and across the coil is 200V

Calculate: a) Impedance, reactance & resistance of coil
b) Power absorbed by the coil
c) Power factor of the coil & circuit
d) Draw phasor diagram

Solution:

Numerical 1 : The voltage applied to a circuit is $v = 100 \sin(\omega t + 30^\circ)$ and the current flowing in the circuit is $i = 15 \sin(\omega t + 60^\circ)$. Find impedance, resistance, reactance, power factor and power consumed.

$$\text{Given: } v = 100 \sin(\omega t + 30^\circ)$$

$$i = 15 \sin(\omega t + 60^\circ)$$

To find: \bar{Z} , R , X , P.f and P

Solution:

$$\textcircled{1} \quad v = V_m \sin(\omega t + \phi)$$

$$v = 100 \sin(\omega t + 30^\circ)$$

$$V_m = 100 \text{ V}, \phi = 30^\circ \rightarrow V_{rms} = \frac{V_m}{\sqrt{2}} = \frac{100}{\sqrt{2}} \text{ V}$$

\textcircled{2} Writing 'v' in Polar form

$$\bar{v} = V_{rms} \angle \phi$$

$$\bar{v} = \frac{100}{\sqrt{2}} \angle 30^\circ \text{ V}$$

$$\bar{v} = V_{rms} \angle \phi$$

$$\textcircled{3} \quad i = I_m \sin(\omega t + \phi) = 15 \sin(\omega t + 60^\circ)$$

$$I_m = 15; I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{15}{\sqrt{2}} \text{ A}$$

\textcircled{4} Writing 'I' in polar form, $\bar{I} = I \angle \phi$

$$\bar{I} = \frac{15}{\sqrt{2}} \angle 60^\circ \text{ A}$$

$$\bar{V} = \bar{I} \bar{Z}$$

$$\textcircled{5} \quad \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{\frac{100}{\sqrt{2}} \angle 30^\circ}{\frac{15}{\sqrt{2}} \angle 60^\circ} = 6.67 \angle -30^\circ \Omega$$

Thinking

$$v = V_{rms} \sin(\omega t + \phi)$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

Polar form

$$\bar{V} = V_{rms} \angle \phi$$

$$\bar{I} = I_{rms} \angle \phi$$

$$\bar{Z} = \frac{\bar{V}}{\bar{I}}$$

$$\bar{Z} = R \pm jX$$

$$R =$$

$$X =$$

$$\text{P.f} = \cos \phi$$

$$P = VI \cos \phi$$

60°

$$⑥ \bar{Z} = (5.776 - j3.33) \Omega \quad \text{P.F. } (0.67, -30)$$

$$\bar{Z} = R \pm jX$$

$$\left\{ \begin{array}{l} \text{i leading V by } 30^\circ \rightarrow \text{ckt is capacitive} \\ \bar{Z} = R - jX_C \end{array} \right.$$

$$⑦ R = 5.77 \Omega$$

$$X_C = 3.33 \Omega$$


$$⑧ \text{P.F.} = \cos \phi = \cos(30^\circ) = 0.868 \text{ (leading)}$$

$$⑨ P = VI \cos \phi = \frac{100}{\sqrt{2}} \times \frac{15}{\sqrt{2}} \times 0.868 = 649.5 \text{ W}$$

Numerical 2 : For the circuit shown in figure below, find current I, voltages V_1 & V_2 and power factor

$$V_1 = IZ_1$$

$$V_2 = IZ_2$$

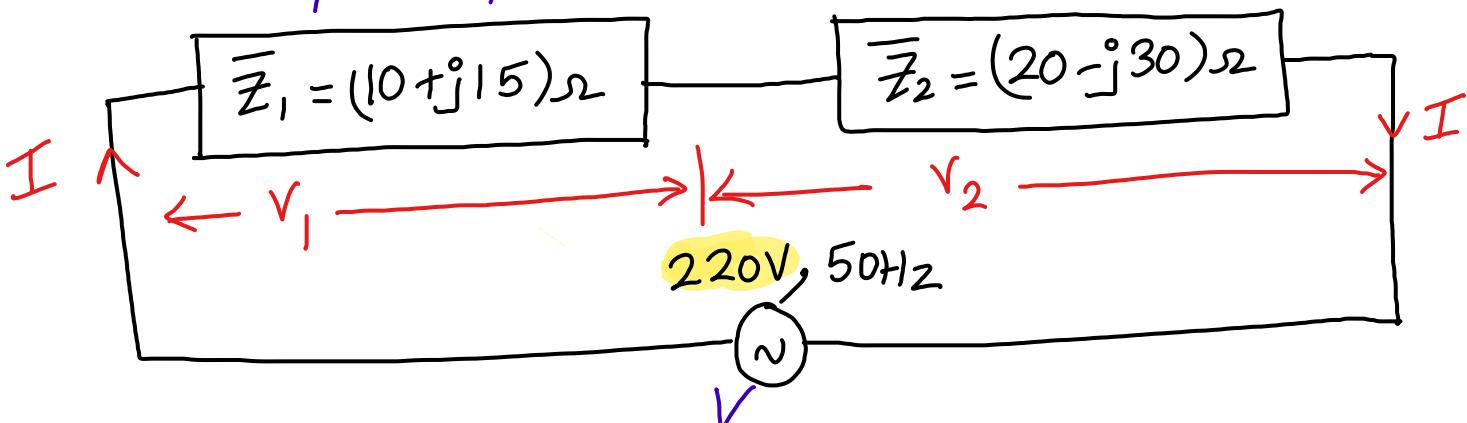

$$\text{Given: } \bar{Z}_1 = (10 + j15) \Omega, V_{\text{rms}} = V = 220 \text{ V}$$

$$\bar{Z}_2 = (20 - j30) \Omega, f = 50 \text{ Hz}$$

To find: I, V_1, V_2 and P.F

$$\text{Solution: } \bar{Z}_1 = 18.03 \angle 56.31^\circ \quad \bar{Z}_2 = 36.05 \angle -56.31^\circ$$

$$① \bar{Z}_1 = 10 + j15 \Omega ; \bar{Z}_2 = 20 - j30 \Omega$$

$$② \bar{Z} = \bar{Z}_1 + \bar{Z}_2 = (30 - 15j) \Omega$$

$$③ \bar{Z} = 33.54 \angle -26.56^\circ \Omega \rightarrow \text{P.F. } (30, -15)$$

$$④ \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{220 \angle 0^\circ}{33.54 \angle -26.56^\circ}$$

Thinking

$$\bar{Z}_1, \bar{Z}_2 \rightarrow \text{given}$$

$$\bar{Z} = \bar{Z}_1 + \bar{Z}_2$$

\bar{Z} in polar form

$$\bar{Z} = Z \angle \phi^\circ \Omega$$

$$\bar{I} = \frac{\bar{V}}{\bar{Z}}$$

$$V_1 = I \bar{Z}_1, V_2 = I \bar{Z}_2$$

$$\text{P.F.} = \cos \phi$$

$$\bar{I} = 6.56 \angle 26.56^\circ A$$

$$\textcircled{5} \quad \bar{V}_1 = \frac{\bar{I}}{\text{polar}} \bar{Z}_1 = (6.56 \angle 26.56^\circ) \times (18.03 \angle 56.31^\circ)$$

$$\bar{V}_1 = 118.27 \angle 82.87^\circ V$$

$$\textcircled{6} \quad \bar{V}_2 = \bar{I} \bar{Z}_2 = (6.56 \angle 26.56^\circ) \times (36.05 \angle -56.31^\circ)$$

$$\bar{V}_2 = 236.48 \angle -29.75^\circ V$$

$$\textcircled{7} \quad P.F = \cos \phi = \cos(26.56^\circ) = 0.894 \text{ leading}$$

Numerical 3 : An inductive coil having inductance of $0.04H$ and resistance of 25Ω has been connected in series with another inductive coil of inductance $0.2H$ and resistance 15Ω . The whole circuit is powered with $230V$, $50Hz$ supply. Calculate the power dissipation in each coil and the total power factor


$$\text{Given: } r_1 = 25\Omega, L_1 = 0.04H$$

$$\text{H.W} \quad r_2 = 15\Omega, L_2 = 0.2H$$

$$V = 230V, f = 50Hz$$

rms value

To find : P_1 , P_2 and $P.F_{total}$

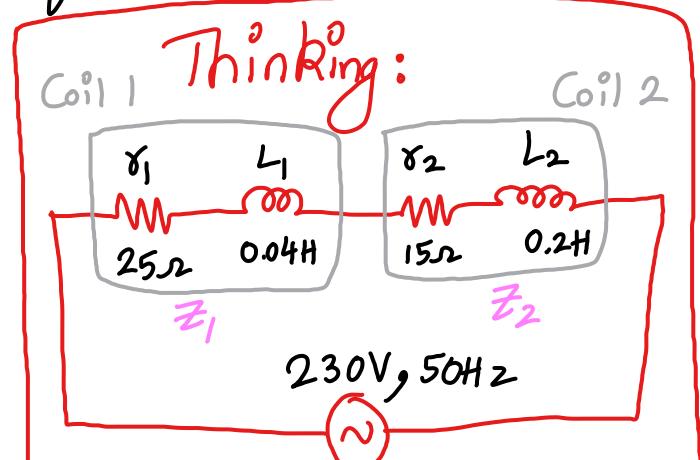

$$\bar{Z}_1 = r_1 + jX_{L1}; \bar{Z}_2 = r_2 + jX_{L2}$$

$$\bar{Z} = \bar{Z}_1 + \bar{Z}_2; I = \frac{\bar{V}}{\bar{Z}}$$

$$P_1 = I^2 r_1, P_2 = I^2 r_2$$

$$P.F = \cos \phi$$

Numerical 4: A capacitor of $35\mu F$ is connected in series with a variable resistor. The circuit is connected across $50\text{Hz}, 230\text{V}$ mains. Find the value of a resistor for a condition when the voltage across the capacitor is half the supply voltage V_C

Given: $C = 35 \times 10^{-6} \text{F}$, $V = 230\text{V}$

$f = 50\text{Hz}$ \leftarrow rms value

$$V_C = \frac{1}{2} V$$

To find: R

Solution:

(a) $X_C = \frac{1}{2\pi f C}$

$$X_C = \frac{1}{2\pi \times 50 \times 35 \times 10^{-6}}$$

$$X_C = 90.947\Omega$$

$$\begin{aligned} V_C &= IX_C \\ V &= IZ \end{aligned}$$

(b) $V_C = \frac{1}{2} V$

$$IX_C = \frac{1}{2} IZ$$

$$Z = 2X_C = 2 \times 90.947\Omega$$


$$Z = 181.89\Omega$$

(3) $Z^2 = R^2 + X_C^2$

$$R^2 = Z^2 - X_C^2 = 181.89^2 - 90.947^2$$

$$R^2 = 24812.6$$

$$R = 157.52\Omega$$

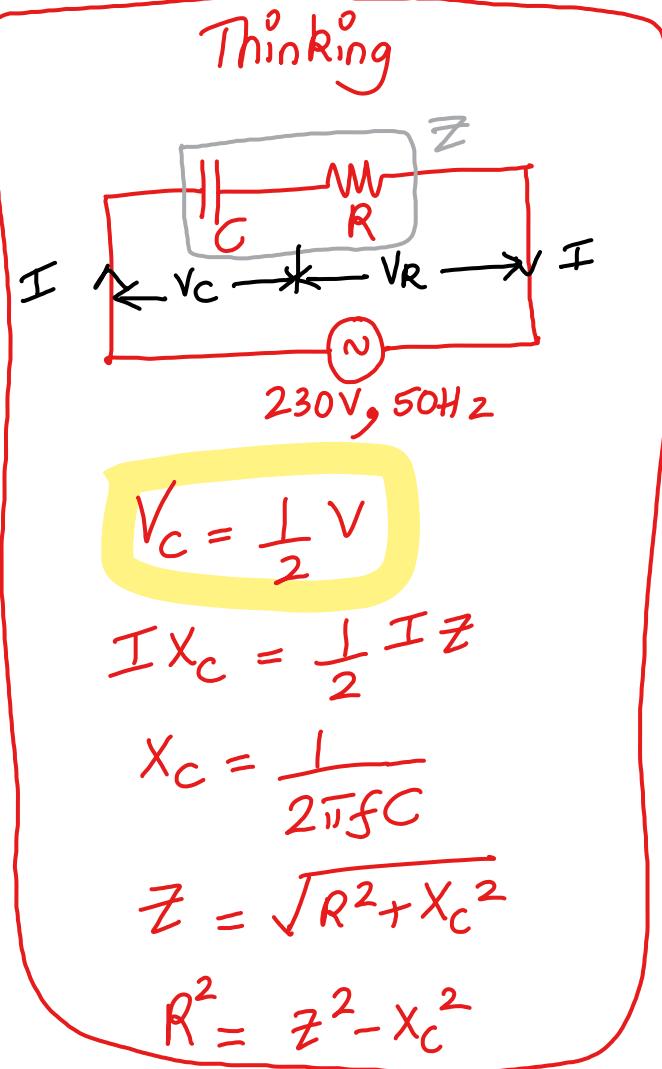

Numerical 5 : A resistance and a capacitance in series is connected across 250V supply draws 5.8A current at a frequency of 60Hz. Find the value of capacitor and also power drawn and power factor. Given resistor value is 20Ω

Given: $R = 20\Omega$, $V = 250V$, $I = 5.8A$, $f = 60\text{Hz}$

Solution:

$$V = IZ$$

① $V = 250V$

$$I = 5.8A$$

$$Z = \frac{V}{I} = \frac{250}{5.8} = 43.103\Omega$$

$$X_C = \frac{1}{2\pi f C}$$

② $Z^2 = R^2 + X_C^2$

$$X_C^2 = Z^2 - R^2 = 43.103^2 - 20^2$$

$$X_C^2 = 1457.86$$

$$X_C = 38.18\Omega$$

③ $X_C = \frac{1}{2\pi f C} \rightarrow C = \frac{1}{2\pi f X_C}$

$$C = \frac{1}{2\pi \times 60 \times 38.18} = 69.4 \mu F$$


④ $\phi = \tan^{-1}\left(\frac{X_C}{R}\right) = \tan^{-1}\left(\frac{38.18}{20}\right)$

$$\phi = 62.35^\circ$$

⑤ $P.f = \cos\phi = \cos(62.35) = 0.4640$, Leading

⑥ $P = VI \cos\phi = 250 \times 5.8 \times 0.464$

P = 672.8 W

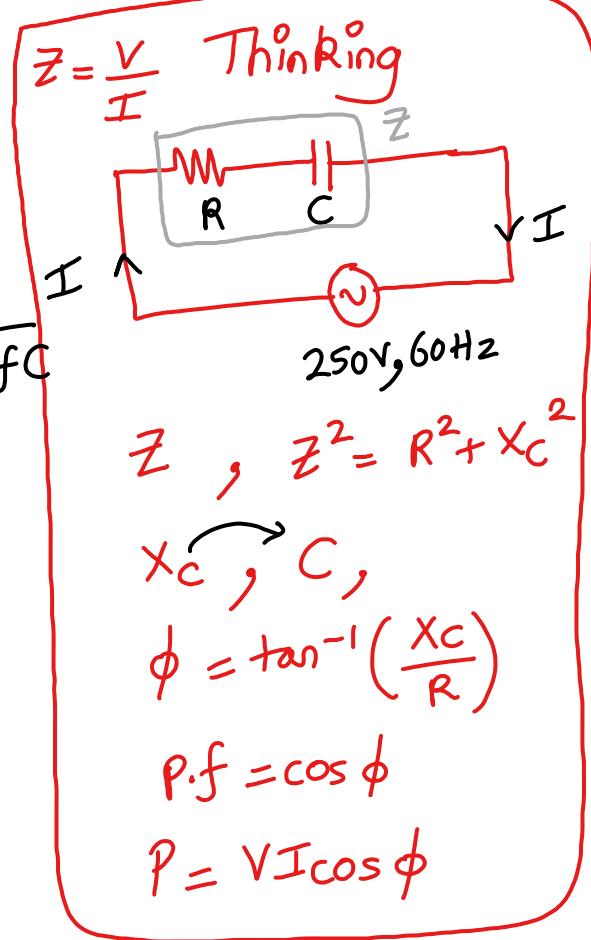

* RLC series circuit:

① Consider an AC circuit containing R , L , C are connected in series across an AC supply

② Let V = rms value of applied voltage

I = rms value of circuit current

Z = impedance of the circuit

③ By ohm's law,


$$V_R = IR ; \text{ where } V_R \text{ is in phase with } I$$

$$V_L = IX_L ; V_L \text{ leads } I \text{ by } 90^\circ$$


$$V_C = IX_C ; V_C \text{ lags behind } I \text{ by } 90^\circ$$

$$V = Iz$$

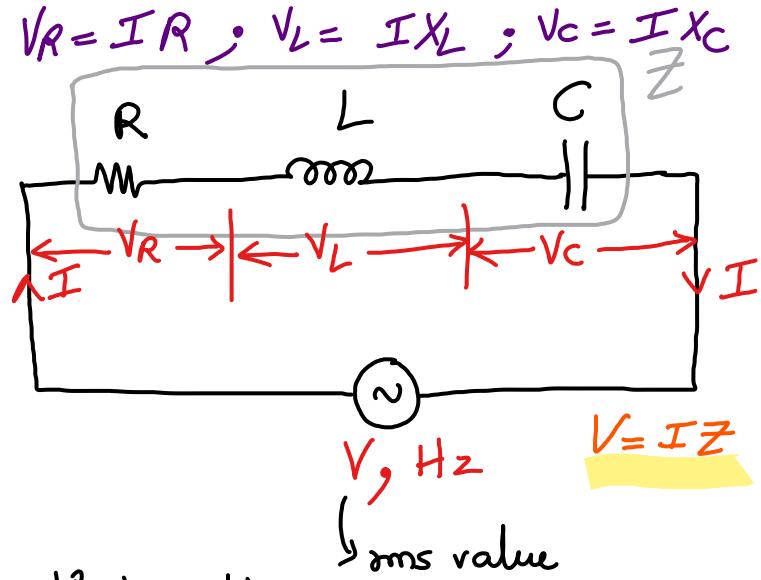④ RLC series circuit can be effectively inductive, capacitive or resistive depending upon the values of X_L and X_C




⑤ Case I : $X_L > X_C$

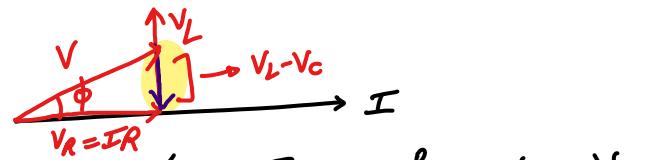

i) If $X_L > X_C \rightarrow$ then $V_C = IX_C$, $V_L = IX_L$ i.e $V_L > V_C$
i.e circuit behaves like an RL series circuit


ii) Phasor diagram ($X_L > X_C$)

a) Taking current as reference point

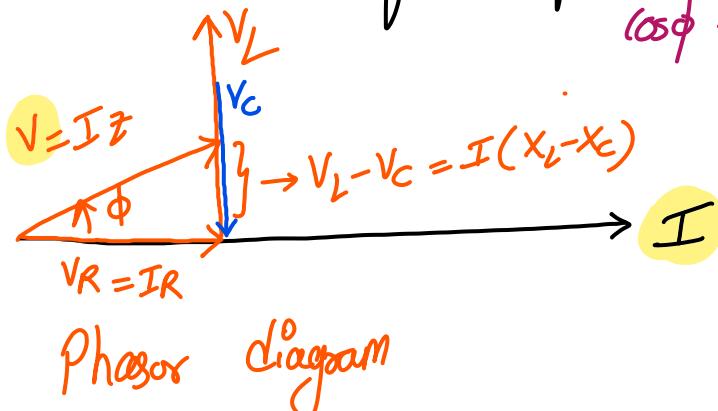

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

$$\cos \phi = \frac{V_R}{V}$$

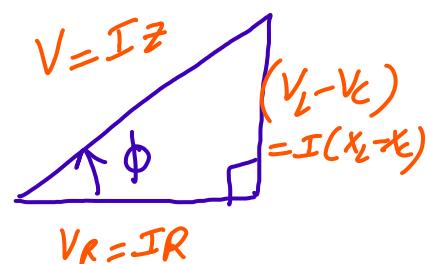

Voltage triangle

b) It is clear from phasor diagram that the current I lags behind the applied voltage V by ϕ ($\phi < 90^\circ$)

c) ∴ Nature of circuit is **Inductive**

d) Phase angle of the circuit,

$$\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right) = \tan^{-1} \left(\frac{I(X_L - X_C)}{IR} \right)$$

Refer voltage triangle


$$\boxed{\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)}$$

e) Power factor,

$$P.f = \cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z}$$

lagging

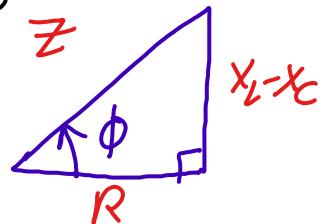iii) Impedance (Z): Dividing each of voltage phasor by 'I' in a voltage triangle \rightarrow we get impedance triangle $Z^2 = R^2 + (X_L - X_C)^2$



a) From impedance triangle,

$$Z^2 = R^2 + (X_L - X_C)^2$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} \quad \Omega$$

Impedance triangle
(when $X_L > X_C$)

b) The impedance can be expressed in rectangular and polar form as,

$$\bar{Z} = [R + j(X_L - X_C)] \Omega \rightarrow \text{Rectangular form}$$

$$\bar{Z} = Z \angle \phi \rightarrow \text{Polar form}$$

where $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$


iv) Power triangle:

$$P = VI \cos \phi = I^2 R$$

$$Q = VI \sin \phi = I^2 X_L$$

$$S = VI = I^2 Z$$

"Power triangle"

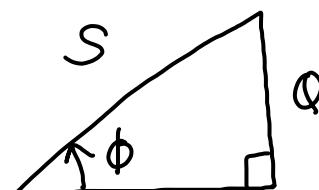

$$(X_L > X_C)$$

$$S^2 = P^2 + Q^2$$




⑥ Case ②: $X_C > X_L$

i) If $X_C > X_L \rightarrow$ then $V_C = IX_C, V_L = IX_L \rightarrow V_C > V_L$

i.e. circuit behaves like an RC series circuit

ii) Phasor diagram ($X_C > X_L$)

a) Taking current as a reference phasor

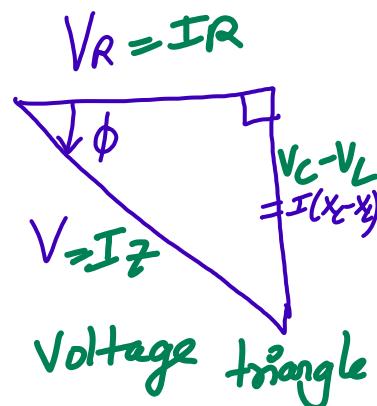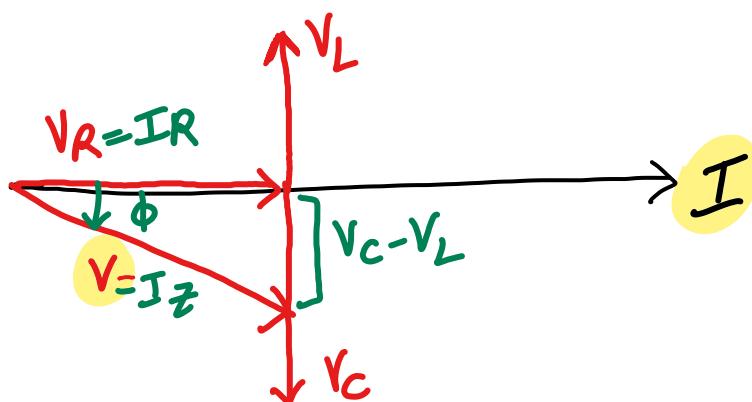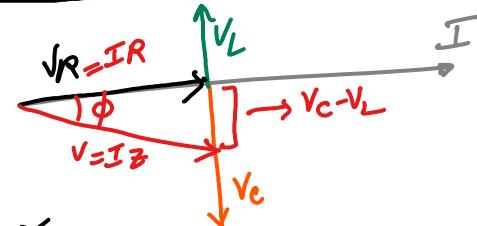

b) It is clear from phasor diagram \rightarrow current I leads the applied voltage V by ϕ ($\phi < 90^\circ$)

c) \therefore Nature of the circuit is Capacitive

d) Phase angle of the circuit

$$\phi = \tan^{-1} \left(\frac{V_C - V_L}{V_R} \right) = \tan^{-1} \left(\frac{I(X_C - X_L)}{IR} \right)$$

$$\boxed{\phi = \tan^{-1} \left(\frac{X_C - X_L}{R} \right)}$$

e) Power factor

$$P.F = \cos \phi = \frac{V_R}{V} = \frac{IR}{IZ} = \frac{R}{Z} \quad \text{leading}$$

iii) Impedance (\bar{Z}): Dividing each of the voltage phasor by I , we get impedance triangle

a) From impedance triangle,

$$\bar{Z}^2 = R^2 + (X_C - X_L)^2$$


$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

b) Circuit impedance (Z) can be expressed in rectangular and polar form as

$$\bar{Z} = R - j(X_C - X_L) \rightarrow \text{Rectangular form}$$

$$\bar{Z} = Z \angle -\phi \Omega \rightarrow \text{Polar form}$$

Impedance triangle
(when $X_C > X_L$)

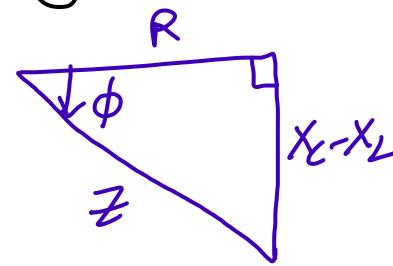


c) Power triangle:

$$S^2 = P^2 + Q^2$$

$$P = VI \cos \phi = I^2 R$$

$$Q = VI \sin \phi = I^2 X_C$$


$$S = VI = I^2 Z$$

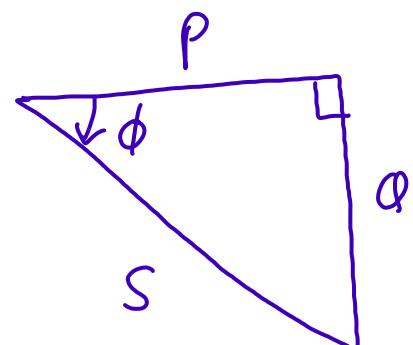

Power triangle
($X_C > X_L$)

—x—

* Analysis of AC Series circuit:

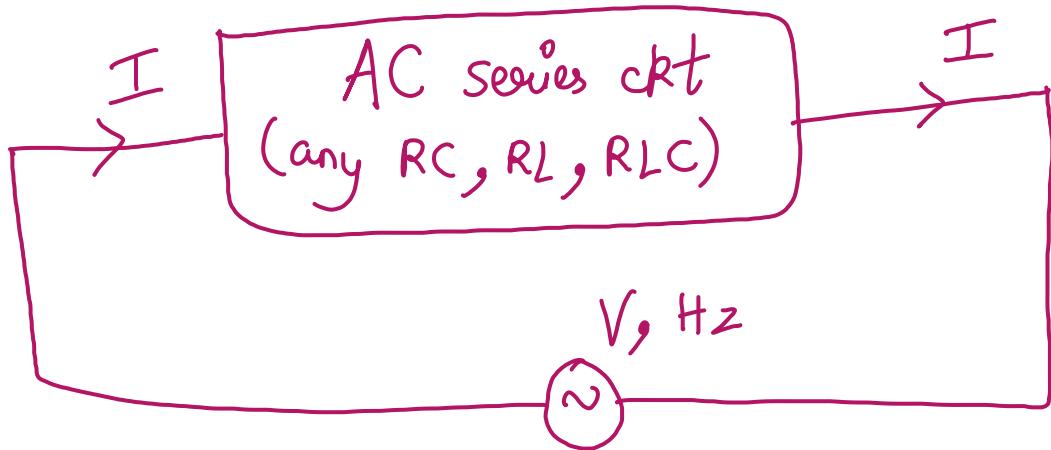

- ① Express circuit impedance (Z) into its rectangular & polar forms

$$\bar{Z} = (R \pm jX) \Omega$$

imaginary part of impedance

total resistance of the circuit

Net reactance of the circuit

- a) If circuit is Inductive $\rightarrow X_L > X_C \rightarrow$ Imaginary part of impedance will be positive
- b) If circuit is Capacitive $\rightarrow X_C > X_L \rightarrow$ Imaginary part of impedance will be negative

② For any unknown AC series circuit

if rectangular form of (Z) is given,

then we get the following information

a) Effective component of circuit

Real part of \bar{Z}

is the total resistive of ckt

Imaginary part of \bar{Z}

is the net reactance of ckt

b) Nature of the circuit

if imaginary part is +ve then ckt is inductive

if imaginary part is -ve then ckt is capacitive

$$\bar{Z} = R + j(X_L - X_C)$$

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

$$Z = (20 - j30)\Omega$$

AC series

V, Hz

\sim

c) Phase angle of the circuit

$$\phi = \tan^{-1} \left(\frac{\text{Imaginary part of } \bar{Z}}{\text{Real part of } \bar{Z}} \right)$$

eg $\bar{Z} = (20 - 30j) \Omega$

a) $R = 20\Omega$, $X = 30\Omega$

b) Nature of ckt is capacitive

c) $\phi = \tan^{-1} \left(\frac{30}{20} \right) = 56.31^\circ$


$$\bar{Z} = Z \angle \phi$$

eg $Z = 10 \angle 45^\circ \Omega$

③ For any unknown AC series circuit

if polar form of Z is given

then we get the following information.

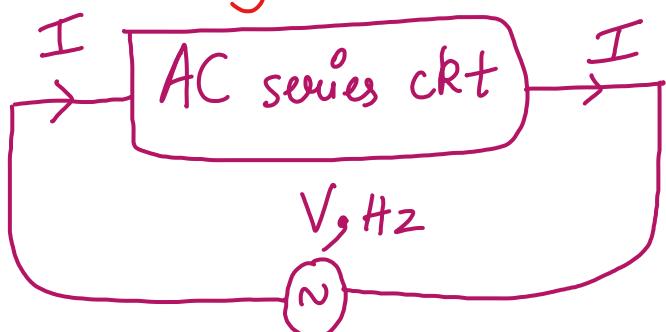


a) Magnitude of impedance Z

b) Phase angle of the circuit

Numerical 2: For the circuit shown below, calculate

- 1) Circuit current
- 2) V_1 & V_2

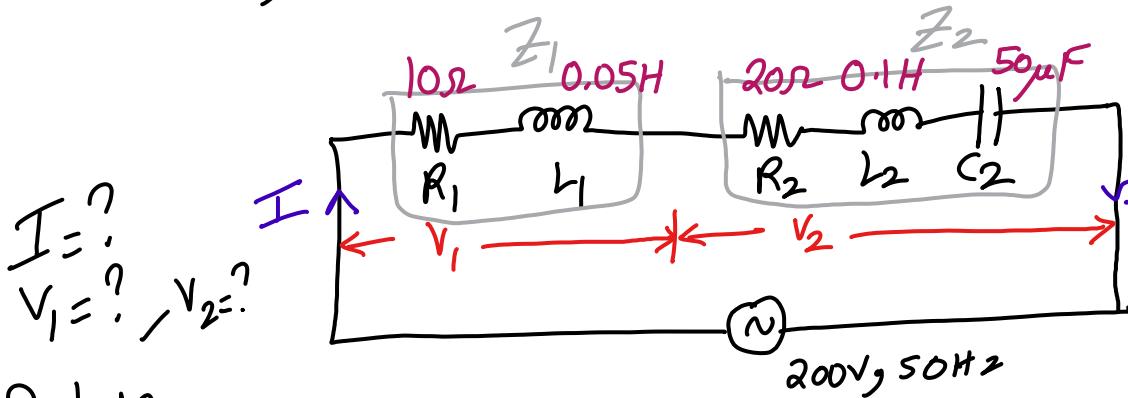

Thinking

- ① $\bar{I} = \frac{\bar{V}}{\bar{Z}}$
- ② \bar{Z}_1
- ③ \bar{Z}_2
- ④ $\bar{V}_1 = \bar{I} \bar{Z}_1$
- ⑤ $\bar{V}_2 = \bar{I} \bar{Z}_2$

Solution:-

$$\textcircled{1} \quad \bar{V} = 200 \angle 0^\circ \text{ V}, \quad R = R_1 + R_2 = 10 + 20 = \underline{30 \Omega}$$

$$\textcircled{2} \quad X_{L1} = 2\pi f L_1 = 100\pi \times 0.05 = \underline{15.7 \Omega}$$

$$\textcircled{3} \quad X_{L2} = 2\pi f L_2 = 100\pi \times 0.1 = \underline{31.42 \Omega}$$

$$\textcircled{4} \quad X_C = \frac{1}{2\pi f C_2} = \frac{1}{100\pi \times 50 \times 10^{-6}} = \underline{63.66 \Omega} \quad X_L = X_{L1} + X_{L2}$$

$\textcircled{5}$ As $X_C > X_L \rightarrow$ circuit is capacitive in nature

$$\textcircled{6} \quad X = X_C - X_L = \underline{16.53 \Omega}$$

$$\textcircled{7} \quad \text{Total impedance: } \bar{Z} = R - jX = (30 - j16.53) \Omega$$

$$\textcircled{8} \quad \bar{Z} = \underline{34.25 \angle -28.85^\circ \Omega} \quad \text{Shift Pol (30, -16.53)}$$

$$\bar{Z} = 34.25 \Omega \quad \phi = -28.85^\circ$$

$$\textcircled{9} \quad \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{34.25 \angle -28.85} = \underline{5.84 \angle 28.85^\circ A}$$

$$\textcircled{10} \quad \bar{Z}_1 = R_1 + jX_1 = 10 + j15.7 \Omega = \underline{18.62 \angle 57.52^\circ \Omega}$$

$$\textcircled{11} \quad \bar{Z}_2 = R_2 - j(X_C - X_{L2}) = 20 - j(63.66 - 31.42)$$

$$\bar{Z}_2 = (20 - j 32.24) \Omega$$

$$\bar{Z}_2 = 37.94 \angle -58.18^\circ$$

$$\textcircled{12} \quad \bar{V}_1 = \bar{I} \bar{Z}_1 = (5.84 \angle 28.85^\circ)(18.62 \angle 57.52^\circ)$$

$$\bar{V}_1 = 108.74 \angle 86.37^\circ V$$

$$\textcircled{13} \quad \bar{V}_2 = \bar{I} \bar{Z}_2 = (5.84 \angle 28.85^\circ)(37.94 \angle -58.18^\circ)$$


$$\bar{V}_2 = 221.57 \angle -29.34^\circ V$$

Numerical 3: A coil of 0.6 power factor in series with a $100\mu F$ connected to 50Hz supply. The voltage across the coil is equal to the voltage across the capacitor. Find inductance & resistance of the coil.

Given: $C = 100\mu F$, $f = 50\text{Hz}$

$P.F_{Coil} = 0.6$, $V_{Coil} = V_C$

To find: L & r ?

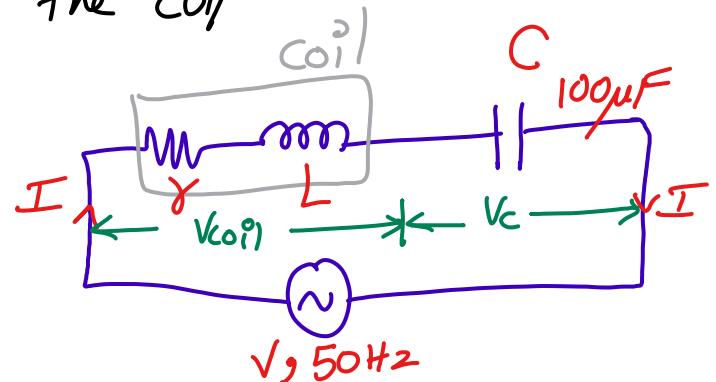

Solution:

$$\textcircled{1} \quad X_C = \frac{1}{2\pi f C} = \frac{1}{100\pi \times 100 \times 10^{-6}}$$

$$X_C = 31.83 \Omega$$

$$\textcircled{2} \quad V_{Coil} = V_C$$

$$\bar{I} \bar{Z}_{Coil} = \bar{I} X_C$$

$$Z_{Coil} = X_C = 31.83 \Omega$$

Thinking

$$\textcircled{1} \quad L = ? \quad X_L = 2\pi f L$$

$$\textcircled{2} \quad Z_{Coil}^2 = r^2 + X_L^2$$

$$\textcircled{3} \quad P.F_{Coil} = \frac{r}{Z_{Coil}}$$

$$\textcircled{4} \quad V_{Coil} = V_C$$

$$\bar{I} \bar{Z}_{Coil} = \bar{I} X_C$$

$$\textcircled{5} \quad X_C = \frac{1}{2\pi f C} \rightarrow$$

$$③ \quad \text{parf}_{\text{coil}} = 0.6 = \frac{\gamma}{Z_{\text{coil}}} \rightarrow \gamma = 0.6 \times 31.83$$

$$\gamma = \underline{19.152}$$

$$④ \quad Z_{\text{coil}}^2 = \gamma^2 + X_L^2$$

$$\rightarrow X_L^2 = Z_{\text{coil}}^2 - \gamma^2 = 31.83^2 - 19.1^2$$

$$X_L^2 = 648.4$$

$$X_L = \underline{25.46 \Omega}$$

$$⑤ \quad Y_L = \frac{1}{2\pi f L} \rightarrow L = \frac{X_L}{2\pi f} = \frac{25.46}{100\pi}$$

$$L = \underline{0.081 \text{ H}}$$

Numerical 4: A resistance R & inductance 0.01 H & a capacitor are connected in series. When a voltage $V = 400 \sin(3000t - 10^\circ) \text{ V}$ is applied to the series combination \rightarrow the current flowing is $10\sqrt{2} \cos(3000t - 55^\circ) \text{ A}$

Find R and C

Solution:


$$V_{\text{rms}} \sin(\omega t + \phi)$$

$$V = 400 \sin(3000t - 10^\circ) \text{ V}$$

$$I = 10\sqrt{2} \cos(3000t - 55^\circ) \text{ A}$$

$$I = 10\sqrt{2} \sin(3000t + 35^\circ) \text{ A}$$

$$I_{\text{rms}} \sin(\omega t + \phi)$$

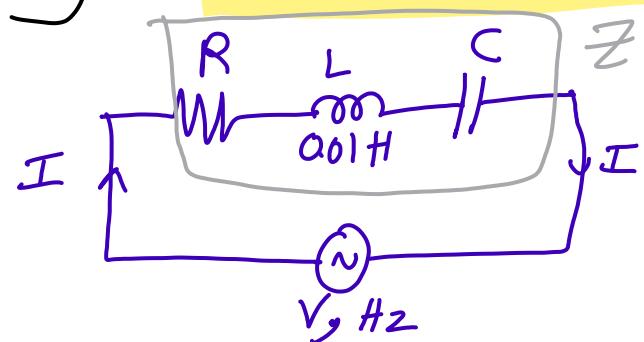

$$V = V_{\text{rms}} \angle \phi$$

$$V_{\text{rms}} = V_{\text{m}} / \sqrt{2}$$

$$I = I_{\text{rms}} \angle \phi$$

$$I_{\text{rms}} = I_{\text{m}} / \sqrt{2}$$

$$① \quad V_{\text{rms}} = V_{\text{m}} / \sqrt{2} = \frac{400}{\sqrt{2}} = 282.84 \text{ V}$$

$$② I_{rms} = \frac{I_m}{\sqrt{2}} = \frac{10\sqrt{2}}{\sqrt{2}} = 10A$$

$$③ \bar{V} = 282.84 \angle -10^\circ V$$

$$\bar{V} = \bar{I} \bar{Z}$$

$$④ \bar{I} = 10 \angle 35^\circ A$$

$$⑤ \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{282.84 \angle -10^\circ}{10 \angle 35^\circ}$$

$$\bar{Z} = 28.284 \angle -45^\circ \Omega$$

$$⑥ \bar{Z} = (20 - j20) \Omega \quad \text{Shift Rec } (28.284, -45)$$

$$\bar{Z} = R - jX$$

$$X = X_C - X_L$$

Capacitive.

$$⑦ R = 20 \Omega$$

$$X = X_C - X_L = 20 \Omega$$

$$⑧ X_L = \omega L = 3000 \times 0.01 = 30 \Omega$$

$$⑨ X_C = X + X_L = 20 + 30 \Omega = 50 \Omega$$


$$⑩ X_C = \frac{1}{\omega C} \rightarrow C = \frac{1}{\omega X_C} = \frac{1}{3000 \times 50}$$

$$C = 6.67 \mu F$$

—x—

Numerical 1: For the circuit shown below,

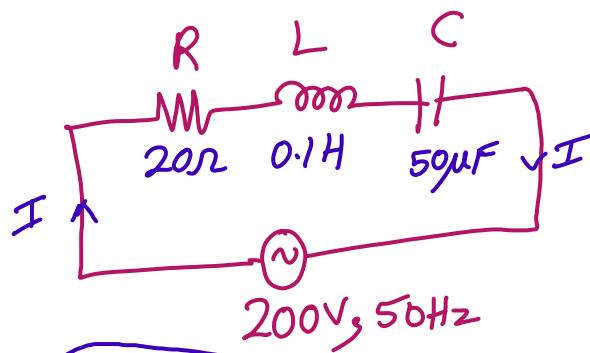- a) Circuit impedance (\bar{Z})
- b) Circuit current (I)
- c) Power factor (P.f)
- d) Active power (P)
- e) Reactive power (Q)
- f) Apparent power (S)



Solution:

$$1) X_L = 2\pi fL = 2\pi \times 50 \times 0.1$$

$$X_L = 31.42 \Omega$$

$$2) X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 50 \times 10^{-6}}$$

$$X_C = 63.66 \Omega$$

$$3) X_C > X_L \rightarrow X = X_C - X_L$$

$$X = 32.24 \Omega$$

Net reactance
Nature of ckt is capacitive

$$4) \bar{V} = 200 \angle 0^\circ V$$

$$5) \bar{Z} = 20 - j32.24$$

$$6) \bar{Z} = 37.94 \angle -58.19^\circ \text{ Pol}(20, -32.24)$$

$$Z = 37.94 \Omega, \phi = -58.19^\circ$$

Thinking

1) Find ckt nature

$$a) X_L = 2\pi fL \quad b) X_C = \frac{1}{2\pi fC}$$

If $X_L > X_C \rightarrow$ inductive
 $X_C > X_L \rightarrow$ capacitive

2) Z in polar form

$$3) \bar{I} = \frac{\bar{V}}{\bar{Z}}$$

$$4) P.f = \cos \phi$$

$$5) P = VI \cos \phi$$

$$6) Q = VI \sin \phi$$

$$7) S = VI$$

$$\bar{Z} = R - jX$$

$$\bar{Z} = Z \angle \phi$$

$$7) \bar{V} = \bar{I} \bar{Z} \rightarrow \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{37.94 \angle -58.19^\circ}$$

$\bar{I} = 5.27 \angle 58.19^\circ$ A

$$8) P.F = \cos \phi = \cos(-58.19) = 0.527 \text{ leading}$$

$$9) P = VI \cos \phi = 200 \times 5.27 \times 0.527 = 555.45W$$

$$10) Q = VI \sin \phi = 200 \times 5.27 \times \sin(-58.19) = -895.69 \text{ VAR}$$

$$11) S = VI = 200 \times 5.27 = 1054 \text{ VA}$$

\overline{x}