

Concept of Admittance:

① Admittance is reciprocal of impedance (\bar{Z})
(Y)

$$\textcircled{2} \quad \bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{R \pm jX}$$

$$\textcircled{i.e.} \quad \bar{Y} = \frac{1}{R \pm jX} \times \frac{R \mp jX}{R \mp jX}$$

$$\textcircled{i.e.} \quad \bar{Y} = \frac{R \mp jX}{R^2 + X^2}$$

$$\textcircled{i.e.} \quad \bar{Y} = \frac{R}{R^2 + X^2} \mp j \frac{X}{R^2 + X^2}$$

$$\textcircled{i.e.} \quad \boxed{\bar{Y} = G \mp jB}$$

Admittance
(\textcircled{Y})
mho

Conductance (\textcircled{G})
(Real part
of \bar{Y})

Susceptance
(\textcircled{B})
(Imaginary
part of \bar{Y})

where,

$$G = \frac{R}{R^2 + X^2}$$

$$B = \frac{X}{R^2 + X^2}$$

③ For RL circuits,

$$\bar{Z} = R + jX_L \longrightarrow Y = G - jB$$

④ For RC circuits,

$$\bar{Z} = R - jX_C \longrightarrow Y = G + jB$$

Parallel AC circuits:

① 'V' is same across each branch


② Current 'I' is different in two branches (I_1, I_2)

③ 3 methods of solving parallel AC circuits

a) By phasor diagram

b) By phasor algebra

c) By Admittance method

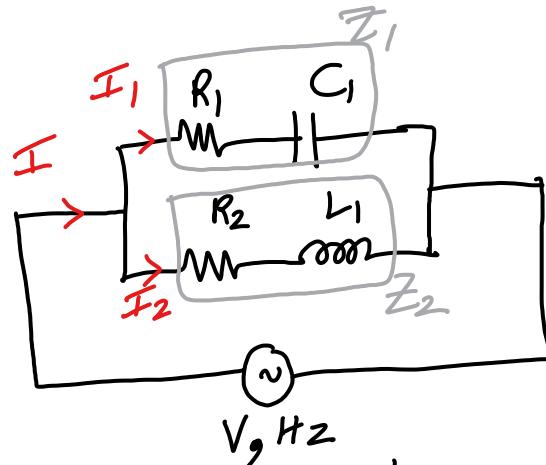



I] Phasor diagram : (applicable for 2 branches)

- a) Find magnitude & phase of each branch current
- b) Draw phasor diagram taking voltage as reference

$$\phi_1 < 90^\circ$$

$$\phi_2 < 90^\circ$$


ϕ -phase angle

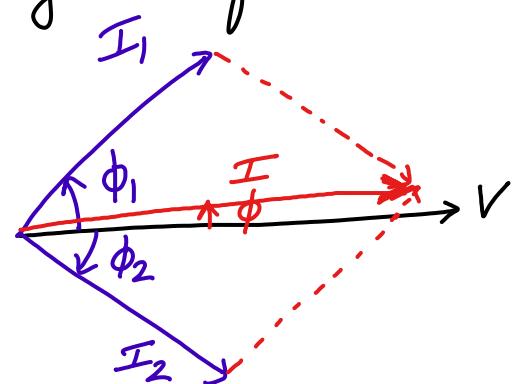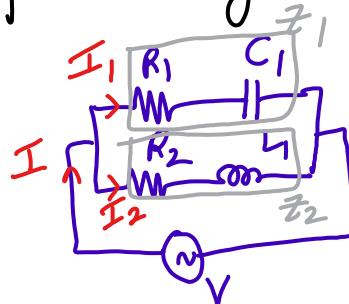

$$i) \bar{Z}_1 = R_1 - jX_C$$

$$\bar{Z}_2 = R_2 + jX_L$$
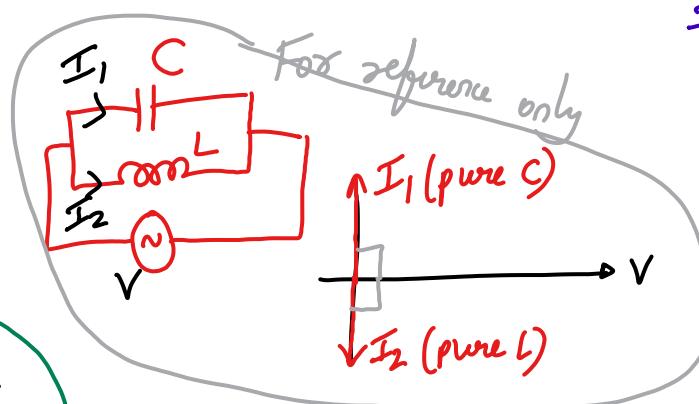
$$\text{mag} \left\{ \begin{array}{l} \bar{Z}_1^2 = R_1^2 + X_C^2 \\ \bar{Z}_2^2 = R_2^2 + X_L^2 \end{array} \right.$$



$$\bar{I} = \bar{I}_1 + \bar{I}_2$$

$$I_1 Z_1 = V = I_2 Z_2$$

$$ii) I_1 = \frac{V}{Z_1} \Rightarrow ; \quad \phi_1 = \tan^{-1} \left(\frac{X_C}{R_1} \right)$$

$$I_2 = \frac{V}{Z_2} \Rightarrow ; \quad \phi_2 = \tan^{-1} \left(\frac{X_L}{R_2} \right)$$

II] Phasor Algebra:

→ Here voltage, current & impedances are expressed in rectangular or polar form

i) $\bar{V} = V - j0 = V \angle 0^\circ$ Volts


ii) $\bar{Z}_1 = R_1 - jX_{C_1} = Z_1 \angle \phi_1$; $Z_1^2 = R_1^2 + X_{C_1}^2$ V, Hz

iii) $\bar{Z}_2 = R_2 + jX_{L_1} = Z_2 \angle \phi_2$; $\phi_1 = \tan^{-1}\left(\frac{X_{C_1}}{R_1}\right)$

iv) $\bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1}$; $\bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2}$; $Z_2^2 = R_2^2 + X_{L_1}^2$; $\phi_2 = \tan^{-1}\left(\frac{X_{L_1}}{R_2}\right)$

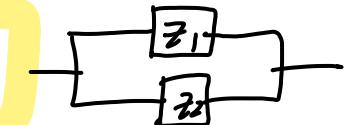v) $\bar{I} = \bar{I}_1 + \bar{I}_2$

$\bar{Z}_{eq} = \bar{Z}_1 \parallel \bar{Z}_2$




III] By admittance method: $\bar{Y} = \frac{1}{\bar{Z}}$

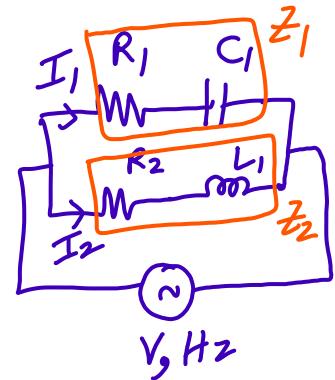a) For given parallel AC ckt,

$$\frac{1}{\bar{Z}_{eq}} = \frac{1}{\bar{Z}_1} + \frac{1}{\bar{Z}_2}$$

i.e $\bar{Y}_{eq} = \bar{Y}_1 + \bar{Y}_2$



$Y_{eq} \rightarrow$ admittance of the ckt

$$\bar{V} = \bar{I} \bar{Z}_{eq}$$

b) Line current

$$\bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}} = \bar{V} \bar{Y}_{eq}$$

c) $\bar{Z}_1 = R_1 - jX_{C_1}$ Ω

$$\bar{Z}_2 = R_2 + jX_{L_1} \Omega$$

$\bar{Y}_1 = (G_1 + jB_{C_1}) \Omega$


$\bar{Y}_2 = (G_2 - jB_{L_1}) \Omega$

B_C - capacitive susceptance


$$G_1 = \frac{R_1}{R_1^2 + X_{C_1}^2}$$

$$G_2 = \frac{R_2}{R_2^2 + X_{L_1}^2}$$
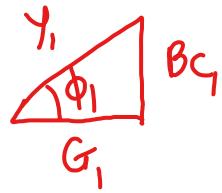
$$B_L \rightarrow \text{Inductive susceptance} \quad B_L = \frac{X_{C_1}}{R_1^2 + X_{C_1}^2}$$



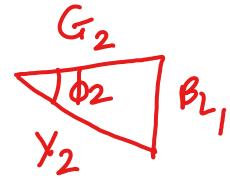
$$B_L = \frac{X_{L_1}}{R_2^2 + X_{L_1}^2}$$



Admittance triangle :

a) For an inductive ckt:

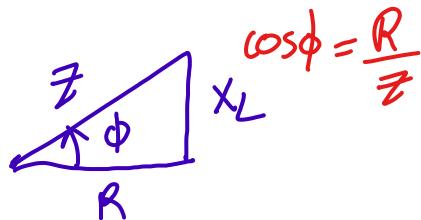


Impedance triangle

$$Z^2 = R^2 + X_L^2$$

$$B_L = Y \sin\phi = \frac{1}{Z} \times \frac{X_L}{Z}$$

$$B_L = \frac{X_L}{Z^2} = \frac{X_L}{R^2 + X_L^2}$$

b) For a capacitive ckt,

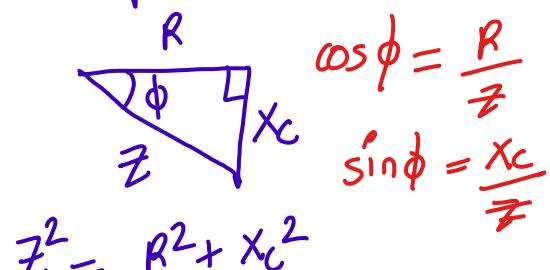


$$Z^2 = R^2 + X_C^2$$

Impedance triangle

$$\text{i)} \quad G = Y \cos\phi = \frac{1}{Z} \frac{R}{Z} = \frac{R}{Z^2} = \frac{R}{R^2 + X_C^2} \quad \checkmark$$
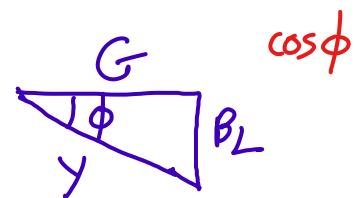
$$\text{ii)} \quad B_C = Y \sin\phi = \frac{1}{Z} \frac{X_C}{Z} = \frac{X_C}{Z^2} = \frac{X_C}{R^2 + X_C^2} \quad \checkmark$$




Admittance triangle

$$Y^2 = G^2 + B_L^2$$


$$G = Y \cos\phi = \frac{1}{Z} \frac{R}{Z}$$
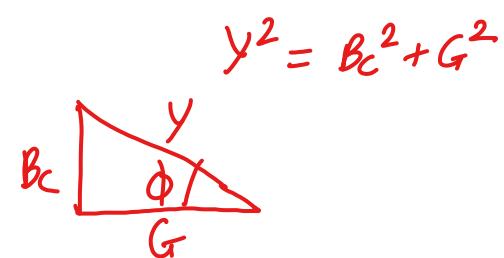
$$G = \frac{R}{Z^2} = \frac{R}{R^2 + X_L^2}$$



Admittance triangle

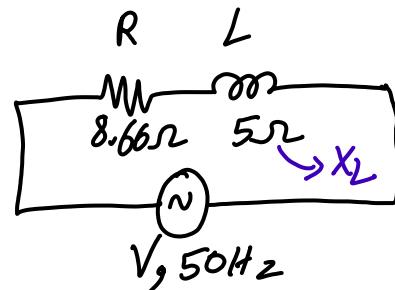Numerical 1: Calculate the admittance & draw the admittance triangle for the circuit shown below



Solution: 1) Circuit impedance

$$\bar{Z} = R + jX_L$$

$$\bar{Z} = 8.66 + j5 \text{ - Rectangular form}$$

$$\bar{Z} = 10 \angle 30^\circ \Omega \quad \text{Shift Pol } (8.66, 5)$$


2) Circuit admittance, $\bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{10 \angle 30^\circ}$

$$\begin{aligned} \bar{Y} &= 0.1 \angle -30^\circ \Omega & \bar{Y} &= Y \angle \phi^\circ \Omega \\ &\text{Polar form of } \bar{Y} && \\ &(Y = 0.1 \Omega, \phi = -30^\circ) && \\ \bar{Y} &= (0.0866 - j0.05) \Omega & \text{Shift Rec } (0.1, -30^\circ) \\ &\text{Rectangular form of } \bar{Y} && \end{aligned}$$

$$\bar{Y} = (G - jB_L) \Omega$$

$$(G = 0.0866 \Omega, B_L = 0.05 \Omega)$$

3) Admittance triangle,

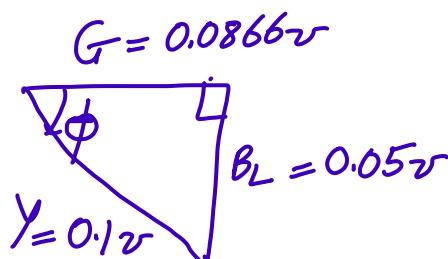

Numerical 2 next

Numerical 2: A resistance of 20Ω & a pure coil of inductance 31.8 mH are connected in parallel across $230V, 50\text{Hz}$ supply. Calculate i) Line current ii) power factor iii) Power consumed by the ckt

Solution:

$$1) \bar{V} = 230 \angle 0^\circ \text{ V}$$

$$2) \bar{Z}_1 = 20 + j0 = 20 \angle 0^\circ \Omega$$

$$3) \bar{Z}_2 = 0 + j10 = 10 \angle 90^\circ \Omega$$

$$4) \bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1} = \frac{230 \angle 0^\circ}{20 \angle 0^\circ} = 11.5 \angle 0^\circ \text{ A}$$

$$\bar{I}_1 = (11.5 + j0) \text{ A}$$

$$5) \bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2} = \frac{230 \angle 0^\circ}{10 \angle 90^\circ} = 23 \angle -90^\circ = (0 - 23j) \text{ A}$$


$$6) \bar{I} = \bar{I}_1 + \bar{I}_2 = (11.5 + j0) + (0 - 23j)$$

$$\bar{I} = (11.5 - 23j) \text{ A} = 25.71 \angle -63.43^\circ \text{ A}$$

$$7) \text{P.f} = \cos \phi = \cos (-63.43^\circ) = 0.447$$

$$8) P = VI \cos \phi = 230 \times 25.71 \times 0.447$$

$$P = 2643.24 \text{ W}$$

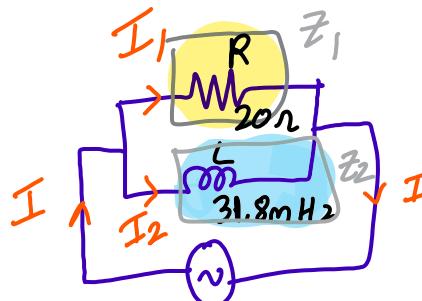

$$Z_1 = R \pm jX$$



$$Z_2 = R \pm jX$$

230V, 50Hz

$$X_L = 2\pi f L$$

$$X_L = 100\pi \times 31.8 \times 10^{-3}$$

$$X_L = 10 \Omega$$

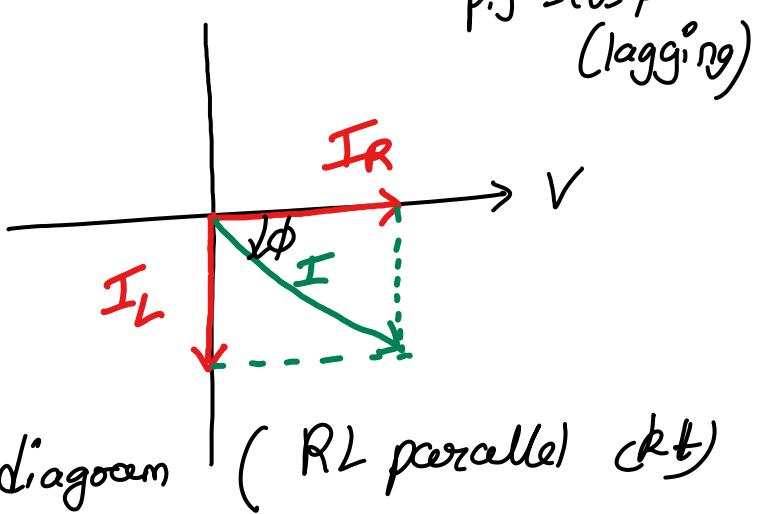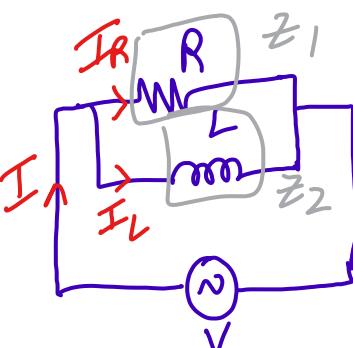

$$\bar{I} = \bar{I}_R + \bar{I}_L$$

$$Z_{eq} = Z_1 \parallel Z_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\frac{1}{Z_{eq}} = \frac{1}{R} + \frac{1}{jX_L}$$

i.e. $\bar{Y} = Y_R - jY_L$


$$\boxed{\bar{Y} = \frac{1}{R} - j\frac{1}{X_L}}$$

$$\bar{Y} = G - jB_L$$

$$\downarrow$$

$$G = \frac{1}{R}; B_L = \frac{1}{X_L}$$

2) RC parallel ckt:

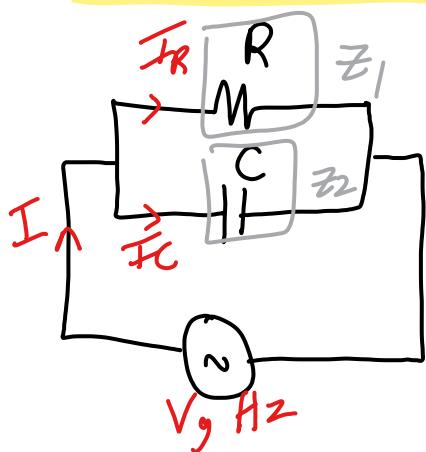

$$\bar{I} = \bar{I}_R + \bar{I}_C$$

$$\bar{Z}_1 = R + j0$$

$$\bar{Z}_2 = 0 - jX_C$$

$$\rightarrow Z_{eq} = Z_1 \parallel Z_2$$

$$\rightarrow \frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$\rightarrow X_{eq} = \frac{1}{R} + \frac{1}{jX_C}$$


$$Y_{eq} = G + jB_C$$

$$P \cdot f = \cos \phi = (\text{leading})$$

$$G = \frac{1}{R}$$

$$B_C = \frac{1}{X_C}$$

$$I_C, I_R, I$$

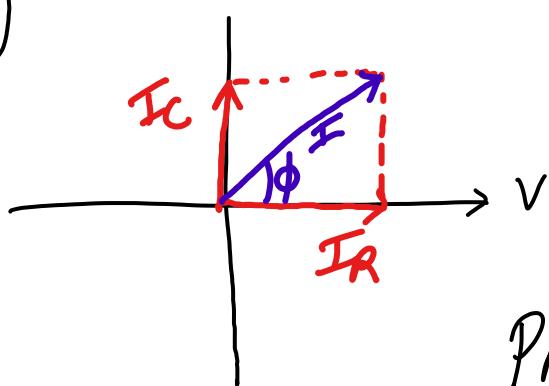


Taken 'V' as reference


Phasor diagram (Parallel RC ckt)

Parallel
RL ac
ckt


RLC parallel AC ckt:

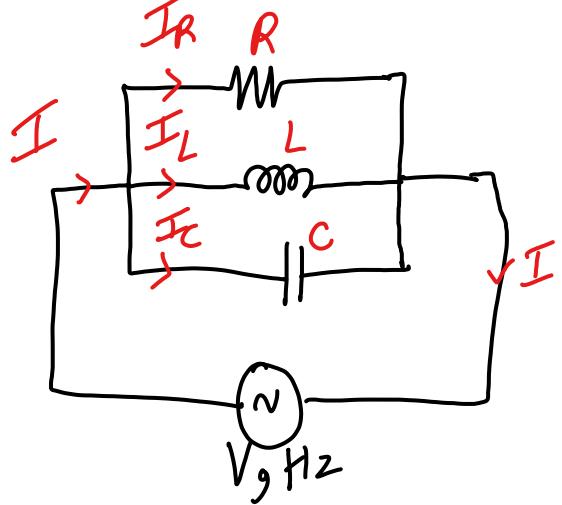

Phasor diagram ($I_L > I_C$)

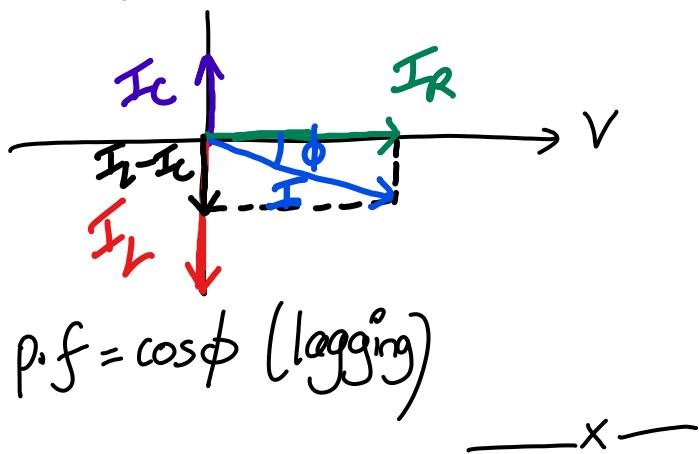
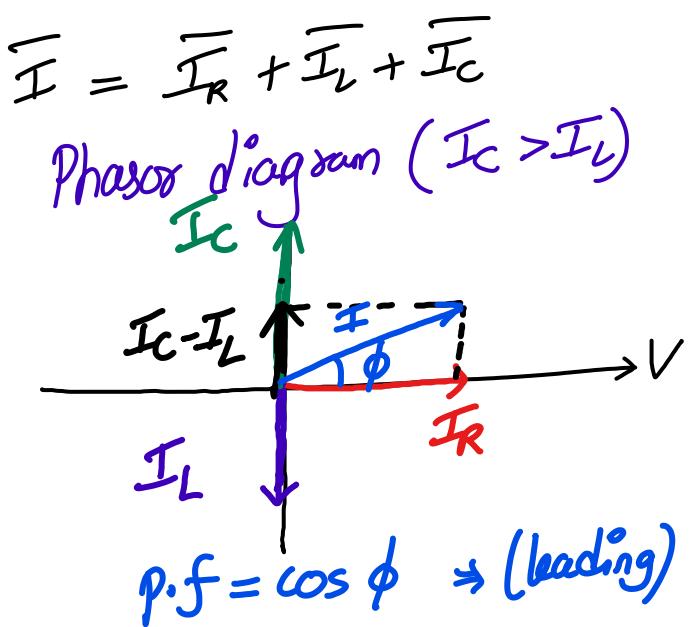
$$\text{p.f} = \cos \phi \text{ (lagging)}$$



$$\text{p.f} = \cos \phi \Rightarrow (\text{leading})$$


Numerical: A coil having a resistance of 50Ω & an inductance of $0.02H$ is connected in parallel with a capacitor of $25\mu F$ across $200V, 50Hz$ supply.

Calculate : a) the current in the coil and capacitor
b) total current drawn and p.f
c) total power consumed by the circuit

Solution: Given $R = 50\Omega, L = 0.02H$

$$V = 200V, f = 50Hz$$

To find : a) I_1 & I_2
b) I & p.f
c) P

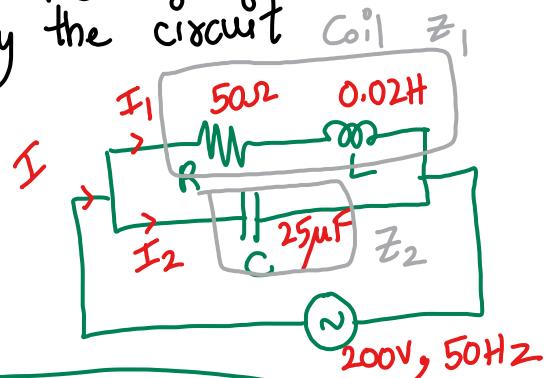

$$\textcircled{1} \quad X_L = 2\pi fL = 100\pi \times 0.02$$

$$X_L = 6.28\Omega$$

$$\textcircled{2} \quad X_C = \frac{1}{2\pi fC} = \frac{1}{100\pi \times 25 \times 10^{-6}}$$

$$X_C = 127.32\Omega$$

$$\textcircled{3} \quad \bar{Z}_1 = R + jX_L = (50 + j6.28)\Omega$$

$$\bar{Z}_1 = 50.39 \angle 7.16^\circ \Omega$$

$$\textcircled{4} \quad \bar{Z}_2 = 0 - jX_C = 0 - j127.32$$

$$\bar{Z}_2 = 127.32 \angle -90^\circ \Omega$$

$$\textcircled{5} \quad \bar{V} = 200 \angle 0^\circ V$$

$$\textcircled{6} \quad \bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1} = \frac{200 \angle 0^\circ}{50.39 \angle 7.16^\circ} = 3.97 \angle -7.16^\circ$$

$$\bar{I}_1 = 3.97 - 0.49j$$

Thinking

a) X_L

b) X_C

c) $\bar{Z}_1 = R + jX_L$

d) $\bar{Z}_2 = 0 - jX_C$

e) \bar{V} in polar form

f) $\bar{I}_1 = \frac{\bar{V}}{\bar{Z}_1}$

$$\bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2}$$

g) $\bar{I} = \bar{I}_1 + \bar{I}_2$

h) $p.f = \cos\phi$

i) $P = \bar{V}\bar{I}\cos\phi$

$$\textcircled{7} \quad \bar{I}_2 = \frac{\bar{V}}{\bar{Z}_2} = \frac{200 \angle 0^\circ}{127.32 \angle -90^\circ} = 1.57 \angle 90^\circ A$$

$$\bar{I}_2 = 0 + 1.57j$$

$$\textcircled{8} \quad \bar{I} = \bar{I}_1 + \bar{I}_2 = (3.94 - 0.49j) + (0 + 1.57j)$$

$$\bar{I} = 3.94 + 1.08j$$

$$\bar{V} \& \bar{I} \rightarrow \phi = 15.33^\circ$$


$$\bar{I} = 4.08 \angle 15.33^\circ A$$

$$\textcircled{9} \quad \text{p.f} = \cos \phi = \cos(15.33) = 0.964$$

$$\textcircled{10} \quad P = VI \cos \phi = 200 \times 4.08 \times 0.964$$

$$P = 786.62 W$$

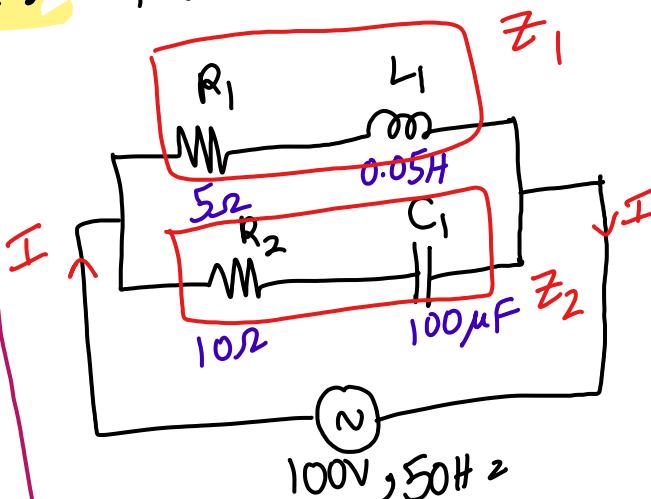Numerical: For the circuit shown below, calculate



Thinking:

- 1) \bar{Z}_1 & \bar{Z}_2
- 2) \bar{Y}_1 & \bar{Y}_2
- 3) \bar{Z}_{eq} & \bar{Y}_{eq}
- 4) $\bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}}$
- 5) $\text{p.f} = \cos \phi$

- a) Impedance & admittance of each branch
- b) Equivalent admittance & impedance of circuit
- c) Supply current & p.f

Solution: 1) $X_{L_1} = 2\pi f L_1 = 100\pi \times 0.05 = 15.71 \Omega$

$$2) X_{C_1} = \frac{1}{2\pi f C_1} = \frac{1}{100\pi \times 100 \times 10^{-6}} = 31.83 \Omega$$

$$3) \bar{Z}_1 = R_1 + jX_{L_1} = (5 + j15.71)\Omega = 16.49 \angle 72.3^\circ \Omega$$

$$4) \bar{Z}_2 = R_2 - jX_{C_1} = (10 - j31.83)\Omega = 33.36 \angle -72.5^\circ \Omega$$

$$5) \bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{16.49 \angle -72.3^\circ} = 0.06 \angle -72.3^\circ \text{ v}$$

$$\bar{Y}_1 = (0.018 - 0.057j) \text{ v}$$

$$6) \bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{33.36 \angle -72.5^\circ} = 0.03 \angle 72.5^\circ \text{ v}$$

$$\bar{Y}_2 = (8.99 \times 10^{-3} + 0.0286j) \text{ v}$$

$$7) \bar{Y}_{eq} = \bar{Y}_1 + \bar{Y}_2 = (0.018 - 0.057j) + (8.99 \times 10^{-3} + 0.0286j)$$

$$\bar{Y}_{eq} = (0.027 - 0.0284j) \text{ v}$$

$$\bar{Y}_{eq} = 0.039 \angle -46.45^\circ \text{ v}$$

$$8) \bar{Z}_{eq} = \frac{1}{\bar{Y}_{eq}} = \frac{1}{0.039 \angle -46.45^\circ} = 25.64 \angle 46.45^\circ$$

$$9) \bar{V} = 100 \angle 0^\circ$$

$$10) \bar{I} = \frac{\bar{V}}{\bar{Z}_{eq}} = \frac{100 \angle 0^\circ}{25.64 \angle 46.45^\circ} = 3.9 \angle -46.45^\circ$$

$$11) p.f = \cos \phi = \cos (-46.45)$$

$$p.f = 0.689$$

$$\bar{I} = I \angle \phi$$

$$\phi = -46.45^\circ$$

— x —

* RLC Series Resonance

① The ability of a radio-receiver to select a certain frequency transmitted by the station & to eliminate frequencies from other stations is based on the 'Principle of Resonance'

- ② In series RLC ckt,
 → X_L causes total current 'I' lags behind the applied voltage 'V'
 → X_C causes total current 'I' leads the applied voltage 'V'

③ When $X_L > X_C \rightarrow$ ckt nature is inductive
 When $X_C > X_L \rightarrow$ ckt nature is capacitive

$$\bar{Z} = R + jX$$


$$\text{⑤ Net reactance } \rightarrow X = |X_L - X_C|$$

$$\text{⑥ } X_L = 2\pi f L \quad ; \quad X_C = \frac{1}{2\pi f C}$$

inductive reactance ($X_L \propto f$)


Supply frequency
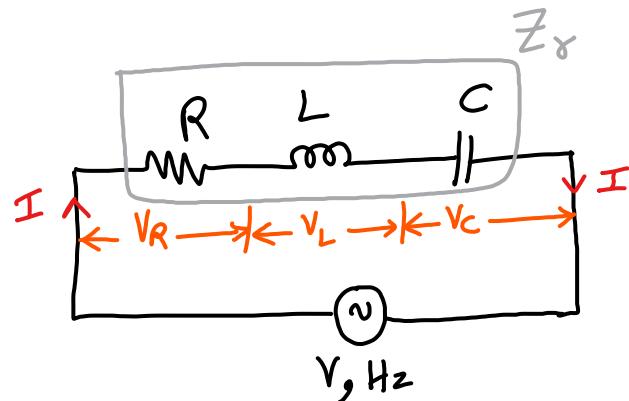
$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$



RLC Series resonant circuit

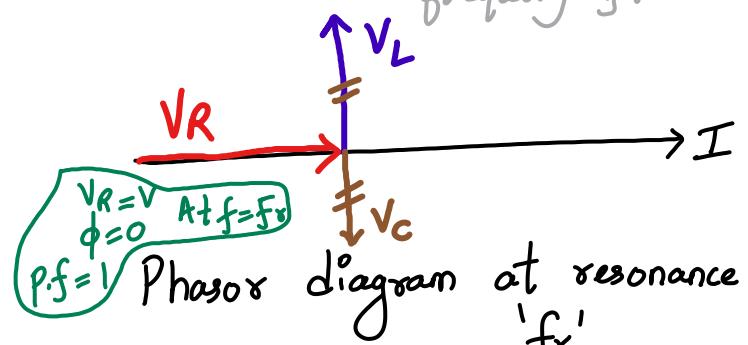Z_r - Circuit impedance at resonance frequency ' f_r '



At resonance,

$$X_L = X_C \quad ; \quad V_R = I_r R$$

$$I_r X_L = I_r X_C$$

$$\rightarrow (V_L = V_C) > V$$

→ Voltage magnification ckt

- ⑦ At resonance frequency ' f_r ' → the inductive reactance becomes equal to capacitive reactance i.e $X_L = X_C$

$$\therefore \text{Net reactance i.e } X = X_L - X_C = 0 \text{ becomes zero}$$

$$Z_r = R + jX = R \Omega$$

⑧ ∵ Impedance 'Z' of the circuit becomes purely resistive (i.e. $Z_r = R$) → At resonance, ($P.f=1$) $\cos\phi = 1$
 $X_L = X_C$, $Z = R + j(X_L - X_C)$ $\phi = 0$ $\rightarrow Z_r = R + j0 = R$ (minimum) $\rightarrow I_r = \frac{V}{Z} = \frac{V}{R}$ (max)

⑨ i.e. Whole ckt behaves as a purely resistive ckt
 i.e. Current 'I' remains in phase with applied voltage V
 i.e. Power factor P.f is unity $P.f = \cos 0 = 1$

⑩ These conditions results in 'Electrical series resonance'

⑪ Effects of Series resonance

a) $X = 0$ i.e. $X_L - X_C = 0$ i.e. $X_L = X_C$

b) Impedance at resonance ' Z_r ' is minimum & is equal to the resistance of the circuit

i.e. $Z_r = R$

c) The current ' I_r ' in the circuit is maximum

i.e. $I_r = \frac{V}{Z_r} = \frac{V}{R}$ A


d) As I_r is maximum → the power absorbed by the ckt will also be at its maximum value $P = I_r^2 R = P_{max}$

⑫ Resonant frequency (f_r): $X_L = \omega L$ $X_C = \frac{1}{\omega C}$

a) X_L & X_C are frequency dependent

b) Higher 'f' → X_L higher & lower X_C

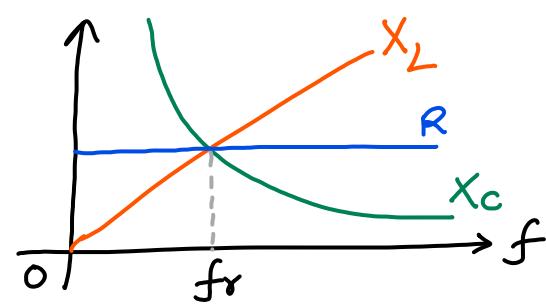c) The frequency at which $X_L = X_C$ in a series RLC ckt is called the 'resonant frequency' (f_r)



⑬ At series resonance, $X_L = X_C$

$$\text{i.e. } 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\text{i.e. } f_r^2 = \frac{1}{4\pi^2 LC}$$

$$\omega_r = 2\pi f_r$$

Resonant frequency

$$\text{i.e. } f_r = \frac{1}{2\pi \sqrt{LC}}$$

in Hz
series RLC resonance

$$\omega_r = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$


⑭ Series Resonance curve:

$$I_r = \frac{V}{R}$$


a) It is a curve between circuit current 'I' and frequency 'f'

b) Current 'I' reaches its maximum value at the resonant frequency 'f_r'

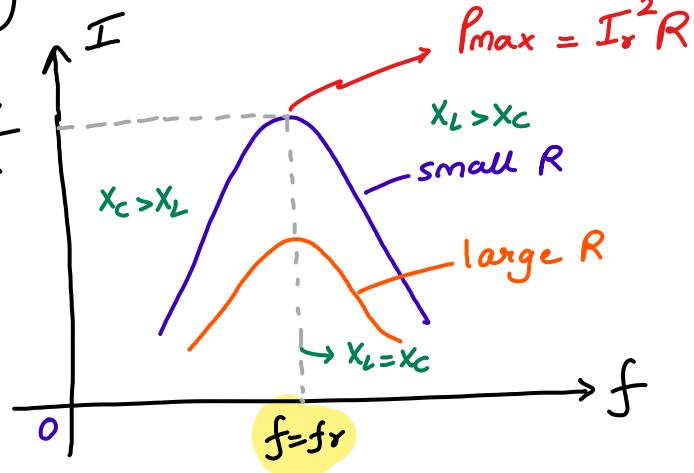c) Current 'I' falls off rapidly on either side since



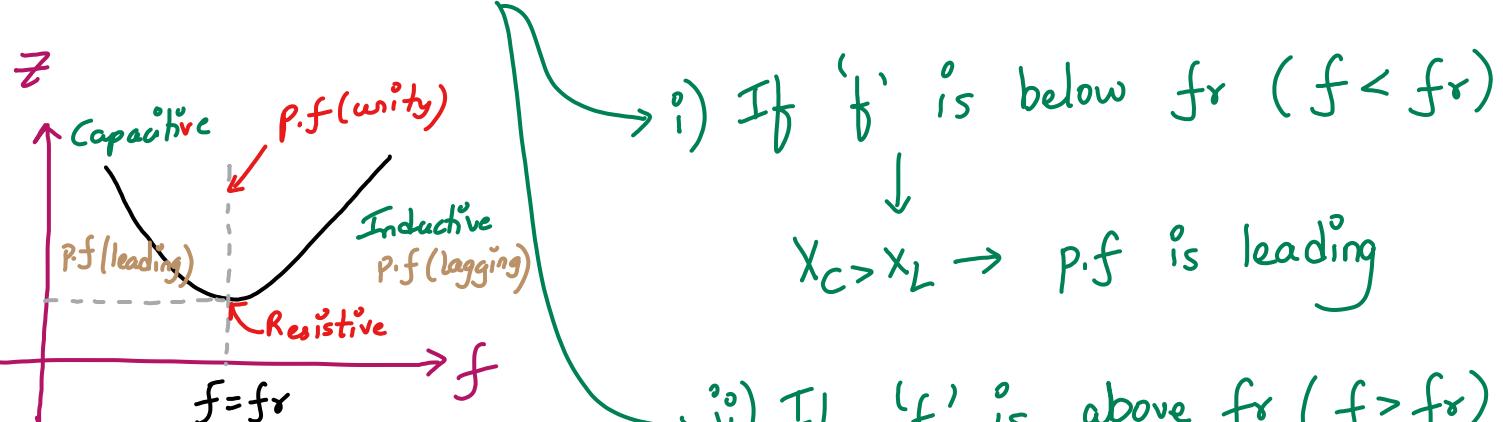Variation of circuit current 'I' with frequency 'f'



i) If 'f' is below f_r ($f < f_r$)

\downarrow
 $X_C > X_L \rightarrow \text{p.f. is leading}$

ii) If 'f' is above f_r ($f > f_r$)

\downarrow
 $X_L > X_C \rightarrow \text{p.f. is lagging}$

$\rightarrow f < f_r \rightarrow \text{Impedance} \rightarrow \text{capacitive, p.f. leading}$

$\rightarrow f = f_r \rightarrow \text{Impedance} \rightarrow \text{resistive, p.f. unity}$

$\rightarrow f > f_r \rightarrow \text{Impedance} \rightarrow \text{inductive, p.f. lagging}$

⑯ Magnitude of current falls rapidly as the frequency 'f' deviates from ' f_r '

⑰ Quality factor (Q-factor) :

a) It is a measure of selectivity/sharpness of series resonant circuit


b) $Q\text{-factor} = \frac{\text{Voltage across } L \text{ & } C \text{ at resonance}}{\text{Voltage across } R \text{ at resonance}} = \frac{V_C \text{ or } V_L}{V_R}$

i.e $Q\text{-factor} = \frac{V_L \text{ or } V_C}{V_R}$ (At resonance,
 $V_R = V$)

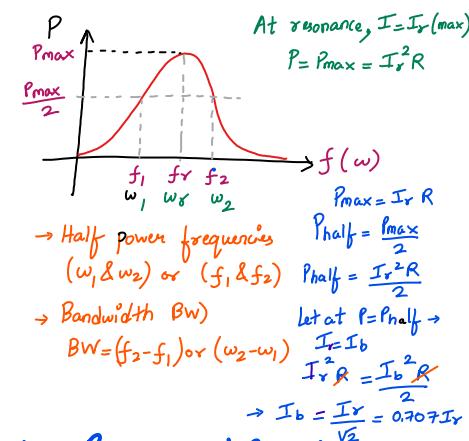c) $\because f_r = \frac{1}{2\pi\sqrt{LC}}$ $\rightarrow Q\text{-factor} = \frac{I_r X_L}{I_r R} = \frac{X_L}{R}$


i.e $Q\text{-factor} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 1 \times L}{2\pi\sqrt{LC} R} = \frac{\sqrt{L} \sqrt{L}}{\sqrt{LC} R}$

i.e $Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$ Series resonant circuit



⑱ Bandwidth of Series RLC resonant circuit:

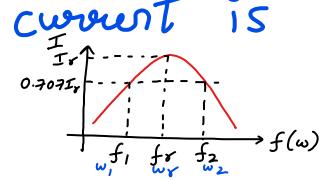a) Bandwidth (Bw) of a series resonance circuit is defined as the range of frequency over which circuit current is equal to 70.7% of its maximum current



b) I_r - Circuit current at resonance

c) $(f_2 - f_1)$ is the bandwidth of the circuit

i.e $BW = f_2 - f_1$ Hz


d) $BW = \frac{R}{2\pi L}$ Hz

→ This can be proven

e) f_1 & f_2 are the limiting frequencies at which current is exactly equal to 70.7% of the maximum value

f) f_1 - lower cut off frequency
 f_2 - higher cut off frequency

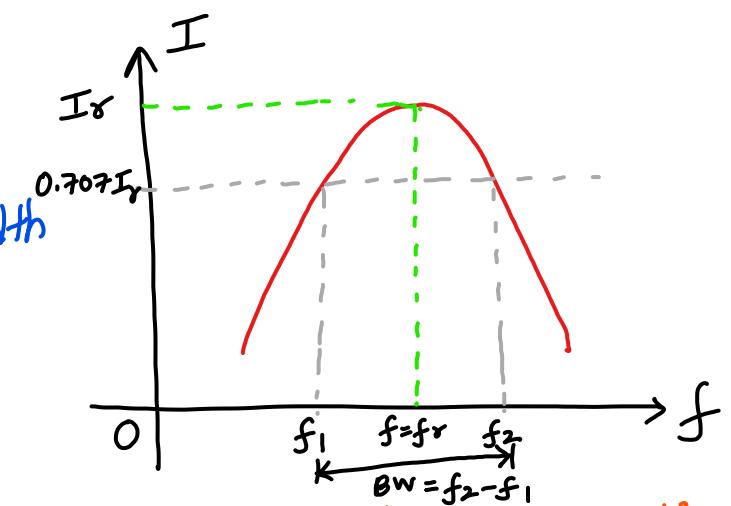g) The resonant frequency is sufficiently centered w.r.t two cut-off frequencies (f_1 & f_2)



Proof: (Only for reading)

① Bandwidth $I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$ - ①

At any frequency $I = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

② At half power point, $I = \frac{I_r}{\sqrt{2}} = \frac{V}{R\sqrt{2}} = \frac{V}{\sqrt{2}R}$ - ②

③ Put ② in eqn ①, $\frac{V}{\sqrt{2}R} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$ $\rightarrow \sqrt{2}R = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

④ Squaring both sides, $2R^2 = R^2 + (\omega L - \frac{1}{\omega C})^2 \rightarrow (\omega L - \frac{1}{\omega C})^2 = R^2$

⑤ $(\omega L - \frac{1}{\omega C}) = \pm R \rightarrow \omega^2 LC - 1 = \pm R \rightarrow \omega^2 LC - 1 = \pm \omega CR$

⑥ $\omega^2 LC - 1 \pm \omega CR = 0 \rightarrow \omega^2 LC - \frac{\omega C}{L} \omega - \frac{1}{LC} = 0$

⑦ $\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0 \rightarrow$ Solving Roots $\omega = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

⑧ Finding roots, $\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$

⑨ For low values of R , $\frac{R^2}{4L^2} \ll \frac{1}{LC}$

⑩ $\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}} \rightarrow \omega = \pm \frac{R}{2L} \pm \frac{1}{\sqrt{LC}}$ - ③

⑪ But, $\omega_r = \frac{1}{\sqrt{LC}}$ $\rightarrow \omega = \pm \frac{R}{2L} \pm \omega_r$ - ④

⑫ Considering ω_r as positive,

$$\omega_1 = \omega_r - \frac{R}{2L}, \quad \omega_2 = \omega_r + \frac{R}{2L}$$

⑬ Bandwidth (BW) $\rightarrow BW = \omega_2 - \omega_1 = \omega_r + \frac{R}{2L} - \omega_r + \frac{R}{2L}$

$$BW = \frac{2R}{2L} = \frac{R}{L} \text{ rad/sec}$$

$$BW \text{ in Hz, } BW = f_2 - f_1 = \frac{\omega_2}{2\pi} - \frac{\omega_1}{2\pi} = \frac{1}{2\pi} (\omega_2 - \omega_1)$$

$$BW = \frac{R}{2\pi L} \text{ Hz} - ⑤$$

⑭ $f_1 = f_r - \frac{R}{4\pi L}, \quad f_2 = f_r + \frac{R}{4\pi L}$

$$f_1 = f_r - \frac{BW}{2}; \quad f_2 = f_r + \frac{BW}{2}$$

$$f_1 = f_r - \frac{BW}{2}$$

$$f_2 = f_r + \frac{BW}{2}$$

$$\omega_1 = \omega_r - \frac{R}{2L} = \omega_r - \frac{BW}{2} = \frac{R}{L} \text{ rad/s}$$

$$\omega_2 = \omega_r + \frac{R}{2L} = \omega_r + \frac{BW}{2}$$

(18) Relation between Q-factor & bandwidth

a) Q factor = $2\pi f_r \frac{L}{R} = \frac{2\pi L}{R} f_r = \frac{f_r}{BW}$

i.e. $f_r = \text{Q-factor} \times BW$

(19) Voltage drop at resonance:

a) At resonance $\rightarrow V_L$ & V_C are equal & antiphase with each other

b) The drop across the resistor (R) V_R is equal to the applied voltage (V)

c) At resonance, $V_R = I_r R = \frac{V}{R} R = V$ i.e. $V_R = V$

$$V_L = I_r X_L = \frac{V}{R} 2\pi f_r L = \frac{V}{R} \cancel{2\pi} \frac{1}{\cancel{2\pi} \sqrt{LC}} L = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_L = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_C = I_r X_C = \frac{V}{R} \frac{1}{2\pi f_r C} = \frac{V}{R} \frac{1}{2\pi} \frac{2\cancel{\pi} \sqrt{LC}}{C} = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_C = \frac{V}{R} \sqrt{\frac{L}{C}}$$

- Numerical 1: A series RLC circuit has the following parameter values: $R = 10\Omega$, $L = 0.014H$, $C = 100\mu F$
- Calculate:
- Resonance frequency ω_r in rad/sec
 - Q-factor Q of the circuit
 - Bandwidth BW in Hz
 - Lower & higher frequency points of the bandwidth V_c
 - Maximum value of the voltage appearing across the capacitor if voltage $v = \sin 1000t$ is applied to series RLC circuit

Given: $R = 10\Omega$, $L = 0.01H$, $C = 100\mu F$, series RLC resonance ckt

To find: a) ω_r b) Q-factor c) BW d) f_1 and f_2
e) V_c

Solution:

$$1) \omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.014 \times 100 \times 10^{-6}}} \text{ rad/sec}$$

$$\omega_r = 845.15 \text{ rad/sec}$$

$$f_r = \frac{\omega_r}{2\pi} = 134.51 \text{ Hz}$$


Thinking

a) $\omega_r = \frac{1}{\sqrt{LC}}$	d) $f_1 = f_r - \frac{BW}{2}$
b) $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$	e) $f_2 = f_r + \frac{BW}{2}$
c) $BW = \frac{R}{2\pi L}$	f) $V_c = \frac{V}{R} \sqrt{\frac{L}{C}}$

$$2) Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.014}{100 \times 10^{-6}}}$$

i.e. $Q\text{-factor} = \underline{1.18}$
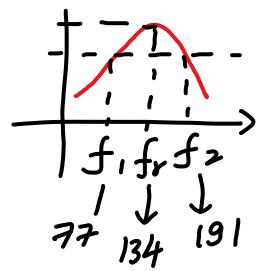
$$3) BW = \frac{R}{2\pi L} = \frac{10}{2\pi \times 0.014} = \underline{113.68} \text{ Hz}$$



$$4) f_1 = f_r - \frac{BW}{2} = 134.51 - \frac{113.68}{2}$$

$$f_2 = f_r + \frac{BW}{2} = 134.51 -$$

$$5) v = \sin 1000t \rightarrow V = \frac{V_m}{\sqrt{2}} = \frac{1}{\sqrt{2}} =$$

6) At resonance \rightarrow voltage that appears across the capacitor is max


$$V_C = \frac{V}{R} \sqrt{\frac{L}{C}} = \frac{0.707}{10} \sqrt{\frac{0.014}{100 \times 10^{-6}}} =$$

$$\underline{V_C =}$$

\downarrow
Numerical ahead

HW: A voltage of $v = 10 \sin \omega t$ is applied to RLC series circuit. At the resonant frequency of the circuit, the maximum value across the capacitor is found to be 500V, BW = 400 rad/sec and impedance at resonance is 100Ω.

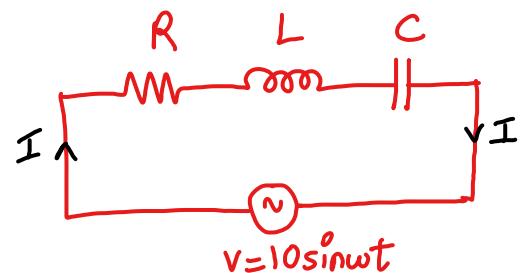- Calculate:
 i) Resonant frequency
 ii) Find the upper & lower limits of BW
 iii) L and C



$$\text{Hint: } 1) v = 10 \sin \omega t, V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$V_C = 500 \text{ V}$$

$$2) \text{BW in Hz} = \frac{\text{BW in rad/s}}{2\pi}$$

$$Z_r = 100 \Omega$$

$$3) Z_r = R \text{ at resonance}$$

$$4) Q\text{-factor} = \frac{V_C}{V}$$

$$5) f_r = \text{BW in Hz} \times Q\text{-factor}$$

$$6) f_1 = f_r - \frac{\text{BW}}{2}$$

$$f_2 = f_r + \frac{\text{BW}}{2}$$

$$7) \text{BW} = \frac{R}{2\pi L} \rightarrow L = \frac{R}{2\pi \times \text{BW}}$$

$$8) f_r = \frac{1}{2\pi \sqrt{LC}} \rightarrow C = ?$$

Answers: $f_r = 4502 \text{ Hz}$

$f_1 = 4470 \text{ Hz}, f_2 = 4533 \text{ Hz}$

$L = 0.25 \text{ H}$


$C = 5 \times 10^{-9} \text{ F}$

Numerical 2 : Determine R, L, C of an RLC series circuit that will resonate at 10 kHz, has a bandwidth of 1000 Hz & draw 15.3 W from 200 V supply, operating at the resonant frequency of the circuit

$$P = \frac{V_R^2}{R} \Rightarrow R? \quad Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$$

Given: $f_r = 10000 \text{ Hz}$, $BW = 1000 \text{ Hz}$,
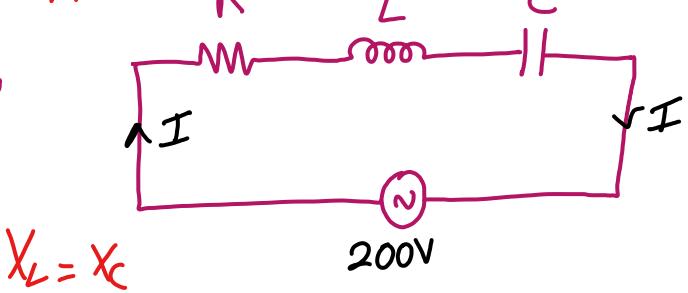
$$P = 15.3 \text{ W}, V_{rms} = 200 \text{ V}$$



$$X_L = X_C$$

To find: R, L and C

Solution:

1) At series resonance, $V_R = V = 200 \text{ volts}$

$$2) P = \frac{V_R^2}{R} \rightarrow R = \frac{V_R^2}{P} = \frac{200^2}{15.3} = \underline{2614.38 \Omega}$$

$$3) Q \text{ factor} = \frac{f_r}{BW} = \frac{10,000}{1000} = \underline{10}$$

$$4) Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R} \rightarrow L = \frac{Q R}{2\pi f_r} = \frac{10 \times 2614.38}{2\pi \times 10 \times 10^3}$$

$$L = \underline{0.416 \text{ H}}$$


5) At resonance, $X_L = X_C$

$$2\pi f_r L = \frac{1}{2\pi f_r C} \rightarrow C = \frac{1}{4\pi^2 f_r^2 L}$$

$$\text{i.e } C = \frac{1}{4\pi^2 \times (10 \times 10^3)^2 \times 0.416}$$

$$\text{i.e } C = \underline{0.609 \times 10^{-9} \text{ F}}$$

$$C = \underline{0.609 \text{ nF}}$$

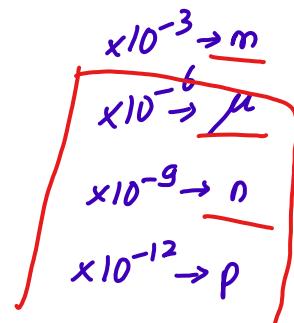

Numerical 3 : A coil having $R = 20\Omega$ and $L = 0.1H$ is connected in series with $C = 50\mu F$. An AC voltage of $250V$ is applied to the circuit. At what value of frequency will the current in the circuit be maximum? What is the value of this current? Also, find V_L and Q-factor

Given: $R = 20\Omega$, $V = 250V$, $L = 0.1H$, $C = 50\mu F$

To find: f_r , V_L , Q-factor, I_r

Solution:

$$1) f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 50 \times 10^{-6}}} \quad \checkmark$$

resonant frequency

$$\text{i.e } f_r = \underline{71.18 \text{ Hz}}$$

2) At series resonance, value of maximum current is,

$$I_r = \frac{V}{R} = \frac{250}{20} = \underline{12.5 \text{ A}}$$


3) $V_L = I_r X_L$

$$\text{i.e } V_L = I_r \times 2\pi f_r L = 12.5 \times 2\pi \times 71.18 \times 0.1$$

$$\text{i.e } V_L = \underline{559.04 \text{ V}}$$

$$4) \text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{20} \sqrt{\frac{0.1}{50 \times 10^{-6}}}$$

$$\text{Q-factor} = \underline{2.236}$$

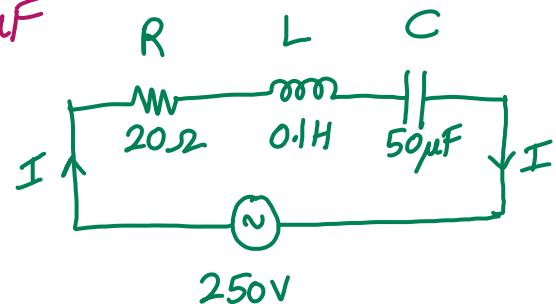


Thinking

$$1) f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$2) I_r = \frac{V}{R}$$

$$3) V_L = I_r X_L$$
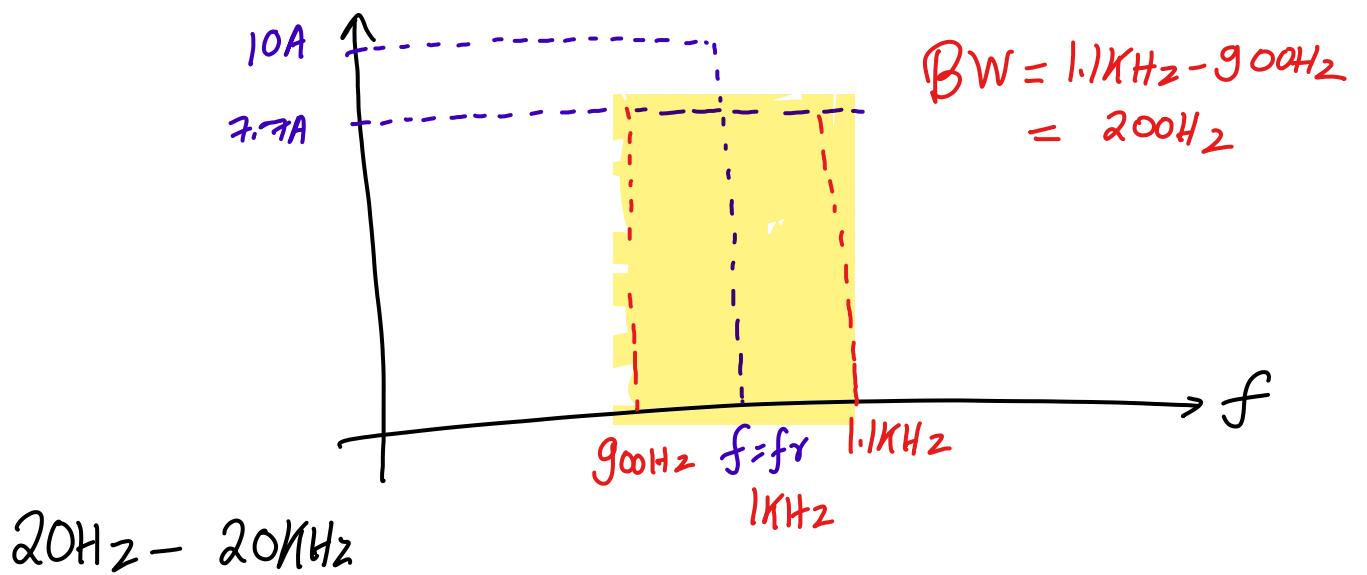
$$4) \text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$



* RLC Series Resonance

① The ability of a radio-receiver to select a certain frequency transmitted by the station & to eliminate frequencies from other stations is based on the 'Principle of Resonance'

- ② In series RLC ckt,
 → X_L causes total current 'I' lags behind the applied voltage 'V'
 → X_C causes total current 'I' leads the applied voltage 'V'

③ When $X_L > X_C \rightarrow$ ckt nature is inductive
 When $X_C > X_L \rightarrow$ ckt nature is capacitive

$$\bar{Z} = R + jX$$


$$\text{⑤ Net reactance } \rightarrow X = |X_L - X_C|$$

$$\text{⑥ } X_L = 2\pi f L \quad ; \quad X_C = \frac{1}{2\pi f C}$$

inductive reactance ($X_L \propto f$)


Supply frequency
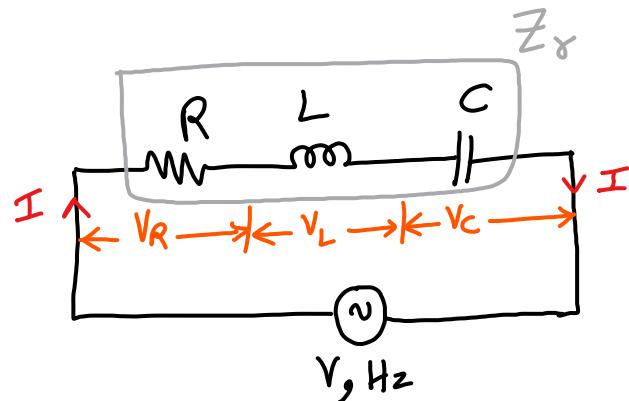
$$\bar{V} = \bar{V}_R + \bar{V}_L + \bar{V}_C$$



RLC Series resonant circuit

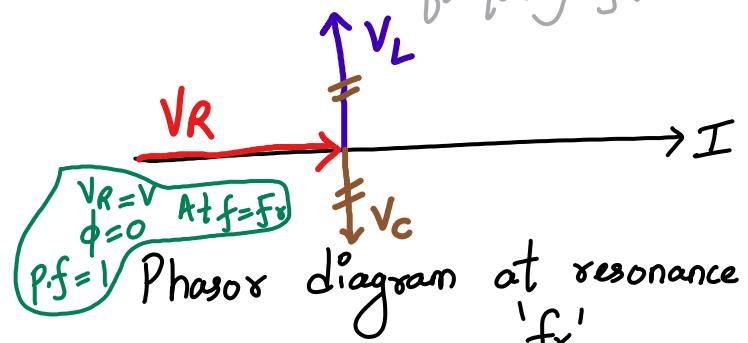Z_r - Circuit impedance at resonance frequency 'fr'



Phasor diagram at resonance 'fr'

At resonance, $X_L = X_C$; $V_R = I_r R$

$$I_r X_L = I_r X_C$$

$$\rightarrow (V_L = V_C) > V$$

→ Voltage magnification ckt

- ⑦ At resonance frequency 'fr' → the inductive reactance becomes equal to capacitive reactance i.e $X_L = X_C$
 \therefore Net reactance i.e $X = X_L - X_C = 0$ becomes zero

$$Z_r = R + jX = R \Omega$$

⑧ ∵ Impedance 'Z' of the circuit becomes purely resistive (i.e. $Z_r = R$) → At resonance, ($P.f=1$) $\cos\phi = 1$
 $X_L = X_C$, $Z = R + j(X_L - X_C)$ $\phi = 0$ $\rightarrow Z_r = R + j0 = R$ (minimum) $\rightarrow I_r = \frac{V}{Z} = \frac{V}{R}$ (max)

⑨ i.e. Whole ckt behaves as a purely resistive ckt
 i.e. Current 'I' remains in phase with applied voltage V
 i.e. Power factor P.f is unity $P.f = \cos 0 = 1$

⑩ These conditions results in 'Electrical series resonance'

⑪ Effects of Series resonance

a) $X = 0$ i.e. $X_L - X_C = 0$ i.e. $X_L = X_C$

b) Impedance at resonance ' Z_r ' is minimum & is equal to the resistance of the circuit

i.e. $Z_r = R$

c) The current ' I_r ' in the circuit is maximum

i.e. $I_r = \frac{V}{Z_r} = \frac{V}{R}$ A


d) As I_r is maximum → the power absorbed by the ckt will also be at its maximum value $P = I_r^2 R = P_{max}$

⑫ Resonant frequency (f_r): $X_L = \omega L$ $X_C = \frac{1}{\omega C}$

a) X_L & X_C are frequency dependent

b) Higher 'f' → X_L higher & lower X_C

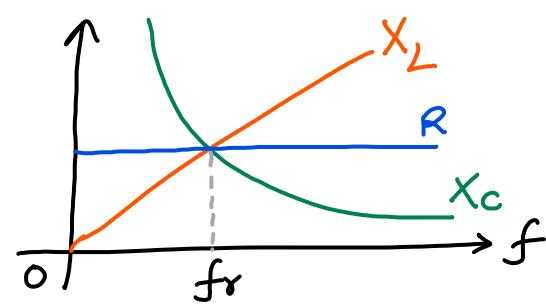c) The frequency at which $X_L = X_C$ in a series RLC ckt is called the 'resonant frequency' (f_r)



⑬ At series resonance, $X_L = X_C$

$$\text{i.e. } 2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$\text{i.e. } f_r^2 = \frac{1}{4\pi^2 LC}$$

$$\omega_r = 2\pi f_r$$

Resonant frequency

$$\text{i.e. } f_r = \frac{1}{2\pi \sqrt{LC}}$$

in Hz
series RLC resonance

$$\omega_r = \frac{1}{\sqrt{LC}} \text{ rad/sec}$$


⑭ Series Resonance curve:

$$I_r = \frac{V}{R}$$


a) It is a curve between circuit current 'I' and frequency 'f'

b) Current 'I' reaches its maximum value at the resonant frequency 'f_r'

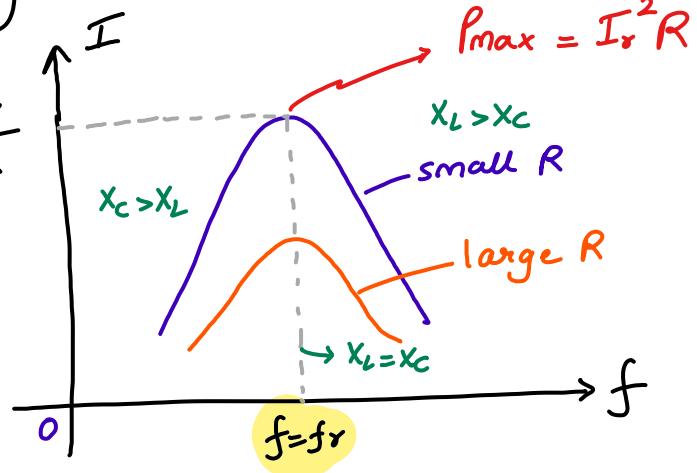c) Current 'I' falls off rapidly on either side since



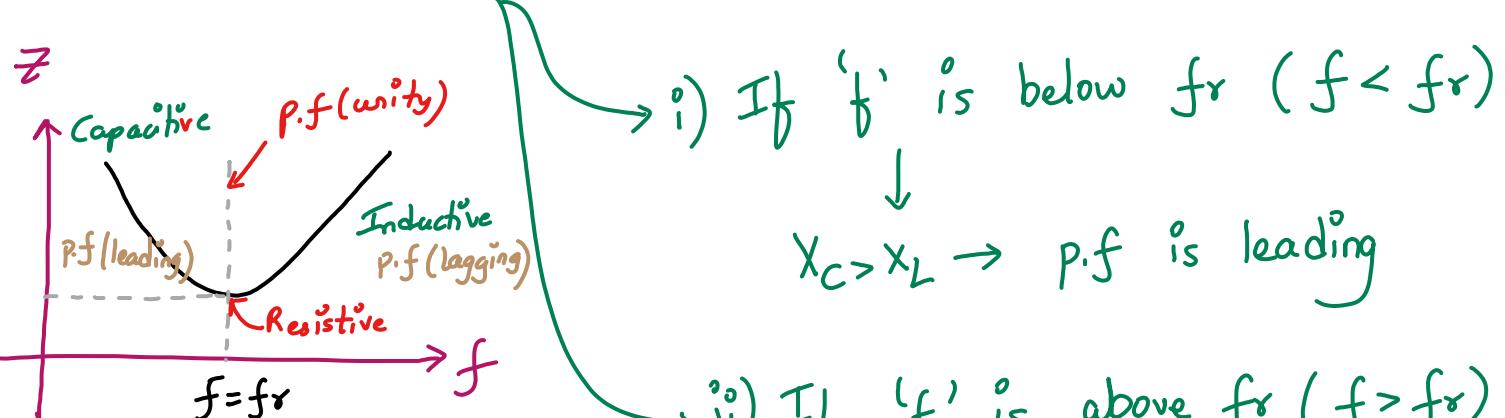Variation of circuit current 'I' with frequency 'f'



i) If 'f' is below f_r ($f < f_r$)

\downarrow
 $X_C > X_L \rightarrow \text{p.f. is leading}$

ii) If 'f' is above f_r ($f > f_r$)

\downarrow
 $X_L > X_C \rightarrow \text{p.f. is lagging}$

$\rightarrow f < f_r \rightarrow \text{Impedance} \rightarrow \text{capacitive, p.f. leading}$

$\rightarrow f = f_r \rightarrow \text{Impedance} \rightarrow \text{resistive, p.f. unity}$

$\rightarrow f > f_r \rightarrow \text{Impedance} \rightarrow \text{inductive, p.f. lagging}$

⑯ Magnitude of current falls rapidly as the frequency 'f' deviates from ' f_r '

⑰ Quality factor (Q-factor) :

a) It is a measure of selectivity/sharpness of series resonant circuit


b) $Q\text{-factor} = \frac{\text{Voltage across } L \text{ & } C \text{ at resonance}}{\text{Voltage across } R \text{ at resonance}} = \frac{V_C \text{ or } V_L}{V_R}$

i.e $Q\text{-factor} = \frac{V_L \text{ or } V_C}{V_R}$ (At resonance,
 $V_R = V$)

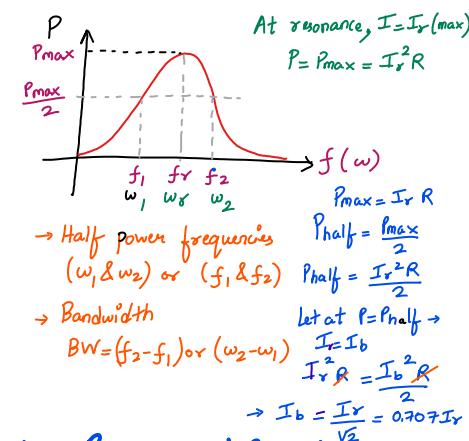c) $\because f_r = \frac{1}{2\pi\sqrt{LC}}$ $\rightarrow Q\text{-factor} = \frac{I_r X_L}{I_r R} = \frac{X_L}{R}$


i.e $Q\text{-factor} = \frac{2\pi f_r L}{R} = \frac{2\pi \times 1 \times L}{2\pi\sqrt{LC} R} = \frac{\sqrt{L} \sqrt{L}}{\sqrt{LC} R}$

i.e $Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$ Series resonant circuit



⑱ Bandwidth of Series RLC resonant circuit:

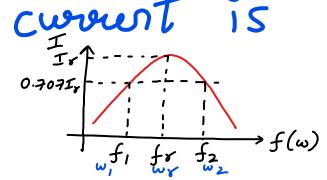a) Bandwidth (BW) of a series resonance circuit is defined as the range of frequency over which circuit current is equal to 70.7% of its maximum current



b) I_r - Circuit current at resonance

c) $(f_2 - f_1)$ is the bandwidth of the circuit

i.e $BW = f_2 - f_1$ Hz


d) $BW = \frac{R}{2\pi L}$ Hz

→ This can be proven

e) f_1 & f_2 are the limiting frequencies at which current is exactly equal to 70.7% of the maximum value

f) f_1 - lower cut off frequency
 f_2 - higher cut off frequency

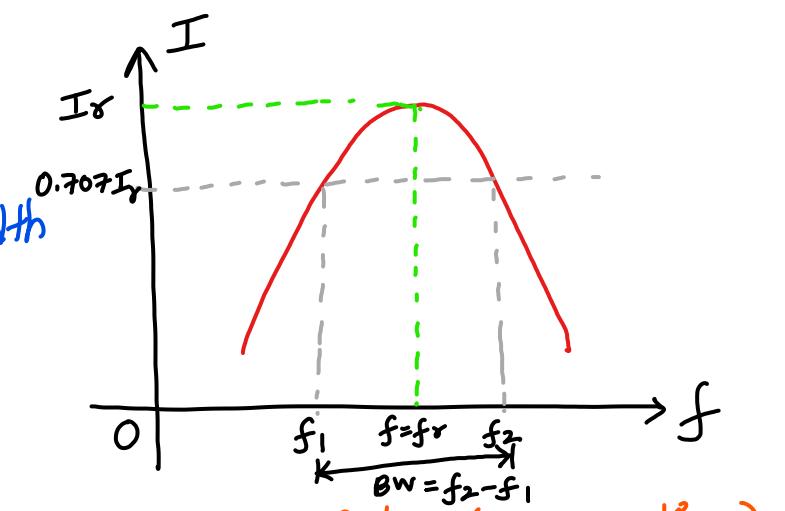g) The resonant frequency is sufficiently centered w.r.t two cut-off frequencies (f_1 & f_2)



Proof: (Only for reading)

① Bandwidth $I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$ - ①

At any frequency $I = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

② At half power point, $I = \frac{I_r}{\sqrt{2}} = \frac{V}{R\sqrt{2}} = \frac{V}{\sqrt{2}R}$ - ②

③ Put ② in eqn ①, $\frac{V}{\sqrt{2}R} = \frac{V}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$ $\rightarrow \sqrt{2}R = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$

④ Squaring both sides, $2R^2 = R^2 + (\omega L - \frac{1}{\omega C})^2 \rightarrow (\omega L - \frac{1}{\omega C})^2 = R^2$

⑤ $(\omega L - \frac{1}{\omega C}) = \pm R \rightarrow \omega^2 LC - 1 = \pm R \rightarrow \omega^2 LC - 1 = \pm \omega CR$

⑥ $\omega^2 LC - 1 \pm \omega CR = 0 \rightarrow \omega^2 LC - \frac{\omega C}{L} \omega - \frac{1}{LC} = 0$

⑦ $\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0 \rightarrow$ Solving Roots $\omega^2 \pm \frac{R}{L} \omega - \frac{1}{LC} = 0$

⑧ Finding roots, $\omega = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$

$$\omega = \frac{-\frac{R}{L} \pm \sqrt{\frac{R^2}{L^2} + \frac{4}{LC}}}{2} = \pm \frac{R}{2L} \pm \sqrt{\frac{R^2}{4L^2} + \frac{1}{LC}}$$

⑨ For low values of R , $\frac{R^2}{4L^2} \ll \frac{1}{LC}$ $f_r = \frac{1}{2\pi\sqrt{LC}}$

⑩ $\omega = \pm \frac{R}{2L} \pm \sqrt{\frac{1}{LC}} \rightarrow \omega = \pm \frac{R}{2L} \pm \frac{1}{\sqrt{LC}}$ - ③

⑪ But, $\omega_r = \frac{1}{\sqrt{LC}}$ $\rightarrow \omega = \pm \frac{R}{2L} \pm \omega_r$ - ④

⑫ Considering ω_r as positive,

$$\omega_1 = \omega_r - \frac{R}{2L}, \quad \omega_2 = \omega_r + \frac{R}{2L}$$

⑬ Bandwidth (BW) $\rightarrow BW = \omega_2 - \omega_1 = \omega_r + \frac{R}{2L} - \omega_r + \frac{R}{2L}$

$$BW = \frac{2R}{2L} = \frac{R}{L} \text{ rad/sec}$$

$$BW \text{ in Hz, } BW = f_2 - f_1 = \frac{\omega_2}{2\pi} - \frac{\omega_1}{2\pi} = \frac{1}{2\pi} (\omega_2 - \omega_1)$$

$$BW = \frac{R}{2\pi L} \text{ Hz} - ⑤$$

$$\omega = 2\pi f$$

⑭ $f_1 = f_r - \frac{R}{4\pi L}, \quad f_2 = f_r + \frac{R}{4\pi L}$

$$f_1 = f_r - \frac{BW}{2}; \quad f_2 = f_r + \frac{BW}{2}$$

$$f_1 = f_r - \frac{BW}{2}$$

$$f_2 = f_r + \frac{BW}{2}$$

$$\omega_1 = \omega_r - \frac{R}{2L} = \omega_r - \frac{BW}{2} \quad \text{rad/s}$$

$$\omega_2 = \omega_r + \frac{R}{2L} = \omega_r + \frac{BW}{2}$$

(18) Relation between Q-factor & bandwidth

a) Q factor = $2\pi f_r \frac{L}{R} = \frac{2\pi L}{R} f_r = \frac{f_r}{BW}$

i.e. $f_r = \text{Q-factor} \times BW$

$$Q = \frac{f_r}{BW}$$

\uparrow
 f_{rL}
 \downarrow
 f_{rc}

(19) Voltage drop at resonance:

a) At resonance $\rightarrow V_L$ & V_C are equal & antiphase with each other

b) The drop across the resistor (R) V_R is equal to the applied voltage (V)

$$V = V_R + V_L + V_C$$

c) At resonance, $V_R = I_r R = \frac{V}{R} R = V$ i.e. $V_R = V$

$$V_L = I_r X_L = \frac{V}{R} 2\pi f_r L = \frac{V}{R} 2\pi \frac{1}{2\pi \sqrt{LC}} L = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_L = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_L = V_C = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_C = I_r X_C = \frac{V}{R} \frac{1}{2\pi f_r C} = \frac{V}{R} \frac{1}{2\pi} \frac{2\pi \sqrt{LC}}{C} = \frac{V}{R} \sqrt{\frac{L}{C}} V$$

$$V_C = \frac{V}{R} \sqrt{\frac{L}{C}}$$

- Numerical 1: A series RLC circuit has the following parameter values: $R = 10\Omega$, $L = 0.014H$, $C = 100\mu F$
- Calculate:
- Resonance frequency ω_r in rad/sec
 - Q-factor Q of the circuit
 - Bandwidth BW in Hz
 - Lower & higher frequency points of the bandwidth V_c
 - Maximum value of the voltage appearing across the capacitor if voltage $v = \sin 1000t$ is applied to series RLC circuit

Given: $R = 10\Omega$, $L = 0.01H$, $C = 100\mu F$, series RLC resonance ckt

To find: a) ω_r b) Q-factor c) BW d) f_1 and f_2
e) V_c

Solution:

$$1) \omega_r = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.014 \times 100 \times 10^{-6}}} \text{ rad/sec}$$

$$\omega_r = 845.15 \text{ rad/sec}$$

$$f_r = \frac{\omega_r}{2\pi} = 134.51 \text{ Hz}$$


Thinking

a) $\omega_r = \frac{1}{\sqrt{LC}}$	d) $f_1 = f_r - \frac{BW}{2}$
b) $Q = \frac{1}{R} \sqrt{\frac{L}{C}}$	e) $f_2 = f_r + \frac{BW}{2}$
c) $BW = \frac{R}{2\pi L}$	f) $V_c = \frac{V}{R} \sqrt{\frac{L}{C}}$

$$2) Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{0.014}{100 \times 10^{-6}}}$$

i.e. $Q\text{-factor} = \underline{1.18}$
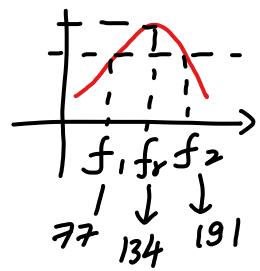
$$3) BW = \frac{R}{2\pi L} = \frac{10}{2\pi \times 0.014} = \underline{113.68} \text{ Hz}$$



$$4) f_1 = f_r - \frac{BW}{2} = 134.51 - \frac{113.68}{2}$$

$$f_2 = f_r + \frac{BW}{2} = 134.51 -$$

$$5) v = \sin 1000t \rightarrow V = \frac{V_m}{\sqrt{2}} = \frac{1}{\sqrt{2}} =$$

$$v = \sqrt{m} \sin \omega t$$

6) At resonance \rightarrow voltage that appears across the capacitor is max

$$V_C = \frac{V}{R} \sqrt{\frac{L}{C}} = \frac{0.707}{10} \sqrt{\frac{0.014}{100 \times 10^{-6}}} =$$


$$\underline{V_C = }$$

An

\downarrow
Numerical ahead

HW: A voltage of $v = 10 \sin \omega t$ is applied to RLC series circuit. At the resonant frequency of the circuit, the maximum value across the capacitor is found to be 500V, BW = 400 rad/sec and impedance at resonance is 100Ω.

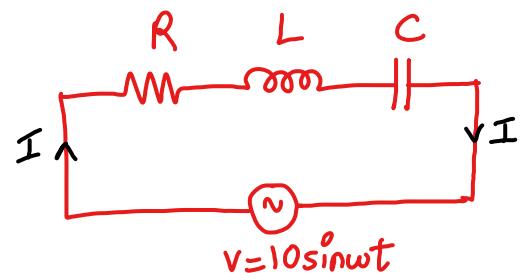- Calculate:
 i) Resonant frequency
 ii) Find the upper & lower limits of BW
 iii) L and C



$$\text{Hint: } 1) v = 10 \sin \omega t, V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

$$V_C = 500 \text{ V}$$

$$2) \text{BW in Hz} = \frac{\text{BW in rad/s}}{2\pi}$$

$$Z_r = 100 \Omega$$

$$3) Z_r = R \text{ at resonance}$$

$$4) Q\text{-factor} = \frac{V_C}{V}$$

$$5) f_r = \text{BW in Hz} \times Q\text{-factor}$$

$$6) f_1 = f_r - \frac{\text{BW}}{2}$$

$$f_2 = f_r + \frac{\text{BW}}{2}$$

$$7) \text{BW} = \frac{R}{2\pi L} \rightarrow L = \frac{R}{2\pi \times \text{BW}}$$

$$8) f_r = \frac{1}{2\pi \sqrt{LC}} \rightarrow C = ?$$

Answers: $f_r = 4502 \text{ Hz}$

$f_1 = 4470 \text{ Hz}, f_2 = 4533 \text{ Hz}$

$L = 0.25 \text{ H}$


$C = 5 \times 10^{-9} \text{ F}$

Numerical 2 : Determine R, L, C of an RLC series circuit that will resonate at 10 kHz, has a bandwidth of 1000 Hz & draw 15.3 W from 200 V supply, operating at the resonant frequency of the circuit

$$P = \frac{V_R^2}{R} \Rightarrow R? \quad Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R}$$

Given: $f_r = 10000 \text{ Hz}$, $BW = 1000 \text{ Hz}$,
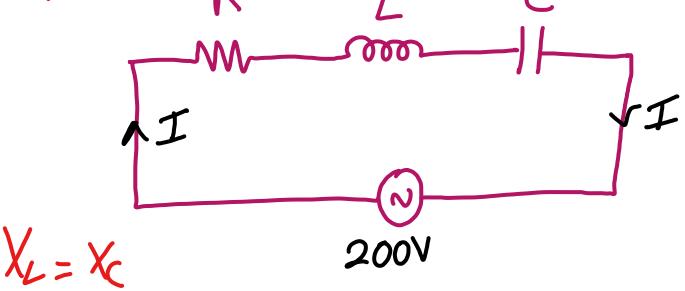
$$P = 15.3 \text{ W}, V_{rms} = 200 \text{ V}$$



$$X_L = X_C$$

To find: R, L and C

Solution:

1) At series resonance, $V_R = V = 200 \text{ volts}$

$$2) P = \frac{V_R^2}{R} \rightarrow R = \frac{V_R^2}{P} = \frac{200^2}{15.3} = \underline{2614.38 \Omega}$$

$$3) Q \text{ factor} = \frac{f_r}{BW} = \frac{10,000}{1000} = \underline{10}$$

$$4) Q = \frac{X_L}{R} = \frac{2\pi f_r L}{R} \rightarrow L = \frac{Q R}{2\pi f_r} = \frac{10 \times 2614.38}{2\pi \times 10 \times 10^3}$$

$$L = \underline{0.416 \text{ H}}$$


5) At resonance, $X_L = X_C$

$$2\pi f_r L = \frac{1}{2\pi f_r C} \rightarrow C = \frac{1}{4\pi^2 f_r^2 L}$$

$$\text{i.e } C = \frac{1}{4\pi^2 \times (10 \times 10^3)^2 \times 0.416}$$

$$\text{i.e } C = \underline{0.609 \times 10^{-9} \text{ F}}$$

$$C = \underline{0.609 \text{ nF}}$$

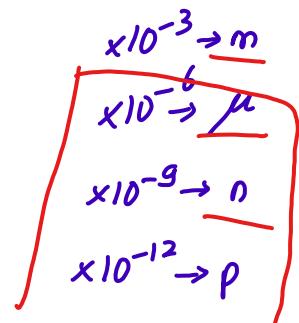

Numerical 3 : A coil having $R = 20\Omega$ and $L = 0.1H$ is connected in series with $C = 50\mu F$. An AC voltage of $250V$ is applied to the circuit. At what value of frequency will the current in the circuit be maximum? What is the value of this current? Also, find V_L and Q-factor

Given: $R = 20\Omega$, $V = 250V$, $L = 0.1H$, $C = 50\mu F$

To find: f_r , V_L , Q-factor, I_r

Solution:

$$1) f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.1 \times 50 \times 10^{-6}}} \quad \checkmark$$

resonant frequency

$$\text{i.e } f_r = \underline{71.18 \text{ Hz}}$$

2) At series resonance, value of maximum current is,

$$I_r = \frac{V}{R} = \frac{250}{20} = \underline{12.5A}$$


3) $V_L = I_r X_L$

$$\text{i.e } V_L = I_r \times 2\pi f_r L = 12.5 \times 2\pi \times 71.18 \times 0.1$$

$$\text{i.e } V_L = \underline{559.04V}$$

$$4) \text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{20} \sqrt{\frac{0.1}{50 \times 10^{-6}}}$$

$$\text{Q-factor} = \underline{2.236}$$

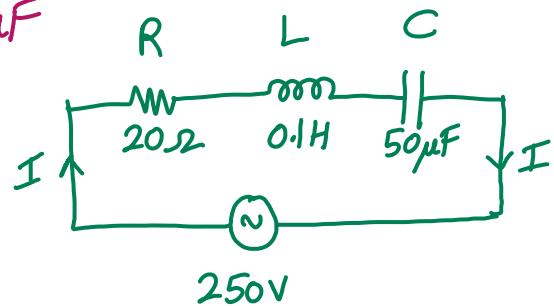

Thinking

$$1) f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$2) I_r = \frac{V}{R}$$

$$3) V_L = I_r X_L$$

$$4) \text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}$$

