

Capacitor Filter: Working and Analysis with waveforms

- In a capacitor filter, the capacitor C_f is connected in parallel with the load R_L as shown in fig 2.1.

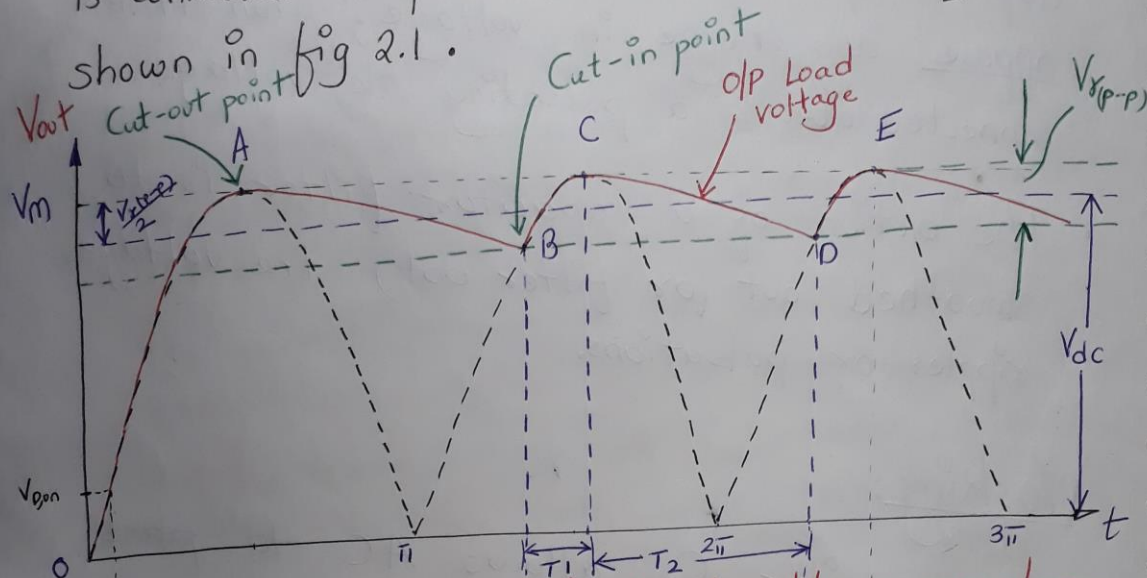


fig 2.2 : Approximate O/P Load-voltage waveforms in a full-wave capacitor-filtered rectifier

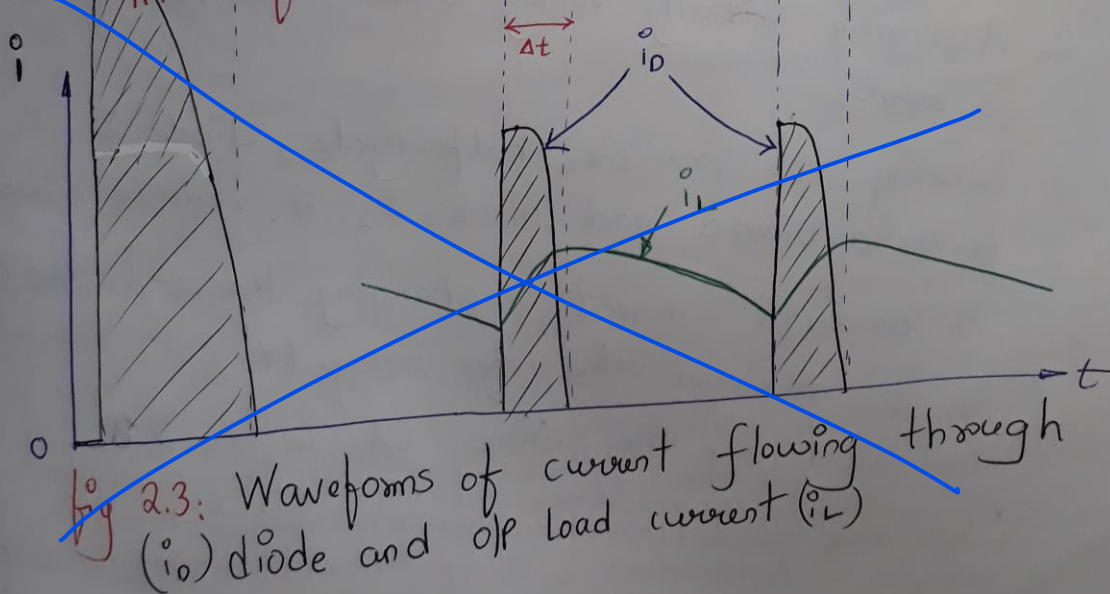


fig 2.3: Waveforms of current flowing through (i_o) diode and o/p load current (i_L)

- The operation of a capacitor filter depends upon the property of a capacitor to oppose any change in voltage, when it is connected across a pulsating dc voltage.
- The action of a capacitor filter is to smoothed out (or filter out) the voltage ripples or pulsations.

Working:

1. The capacitor C_1 allows AC to pass through it whereas it blocks DC.
2. Assuming initially voltage across capacitor C_1 is zero.
3. During the positive half cycle, diode D_1 is forward-biased and diode D_2 is reverse-biased. D_1 conducts current, charging the capacitor C_1 to its maximum value of voltage (V_m) as indicated by the curve OA in fig 2.2.

• Since there is no resistance in the charging path, except diode forward resistance (which is small), the charging is instantaneous i.e. charging time is v. small.

4. After point A, the ac input voltage begins to decrease, but capacitor C_1 is already charged to the value V_m . 17
5. But since voltage across the capacitor C_1 cannot change immediately, therefore after point A, capacitor voltage (V_{C_1}) is more than the input voltage. (which means cathode voltage of the diode D_1 is more than anode voltage) Hence, diode D_1 is reverse biased in the positive half cycle itself.
6. Hence, charging of C_1 is stopped and now capacitor C_1 starts discharging slowly through the load resistor (R_L), thus the o/p Load voltage (V_{out}) decreases by a small value.
 (Discharging time constant $\tau_d = C_1 R_L$ is much greater than charging time constant $\tau_c = C_1 R_f$) $R_f \rightarrow$ forward resistance of diode $D_1 \rightarrow$ v. small.
7. At the same time positive half cycle is over and negative half-cycle begins.

- Now diode D_1 continues to be in reverse bias. Next diode D_2 is also still reverse-biased due to voltage across capacitor.

8. Therefore, capacitor C_1 continues to discharge and reaches the point B as shown by section A-B in fig 2.2

9. After point

9. At point B in the waveform, the instantaneous voltage of the rectified o/p is greater than the capacitor voltage, thus diode D_2 is forward-biased and starts charging the capacitor upto the peak voltage V_m as shown by section B-C in fig 2.2.

10. This process repeats during subsequent cycle and we get a "filtered" o/p as shown in the fig 2.2.

11. In the waveforms (fig 2.2), at point A, diode stops conducting, hence it is known as 'cut-out' point / cut-off point.

• At point B, diode starts conducting, hence it is known as 'cut-in point'. 19

12. The output load voltage V_{out} is almost a DC voltage with small ripple voltage (V_{r-p-p}) as shown in fig 2.2.

The ripple (i.e. ac component) present in the o/p voltage of a capacitor filter is due to charging and discharging of a capacitor.

13. The smaller the ripple voltage (V_{r-p-p}), the better is the filtering action.

14. One way to reduce the ripple is by increasing the discharging time constant which is equal to $R_L \cdot C$.

15. Figure (2.3) shows waveforms of current flowing through the diode (i_D) and o/p load current (i_L). During the charging time (from point B to point C), the rectifier supplies the charging current I_C