

Diode application : Rectifier

Half-wave rectifier


Full-wave center tap rectifier

Full-wave bridge rectifier

+ Filters (Capacitor filter)
only with 'R' load

- ① Ckt diagram
 - ② Working
 - ③ I_{p-olp} w.r.t time
 - ④ Analysis :-
- | | |
|----------------------------------|--------------------------|
| a) V _{out avg} | { I _{out avg} } |
| b) V _{out rms} | { I _{out rms} } |
| c) Rectific ⁿ eff (%) | |
| d) Ripple factor (%) | |
| e) TUF | |

Diode basics:-

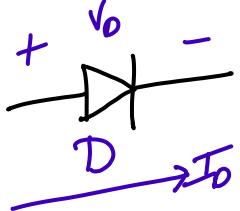

D. is F.B (ON)




D. is R.B (OFF)



Half-wave Rectifier with 'R' load:




Circuit diagram:-

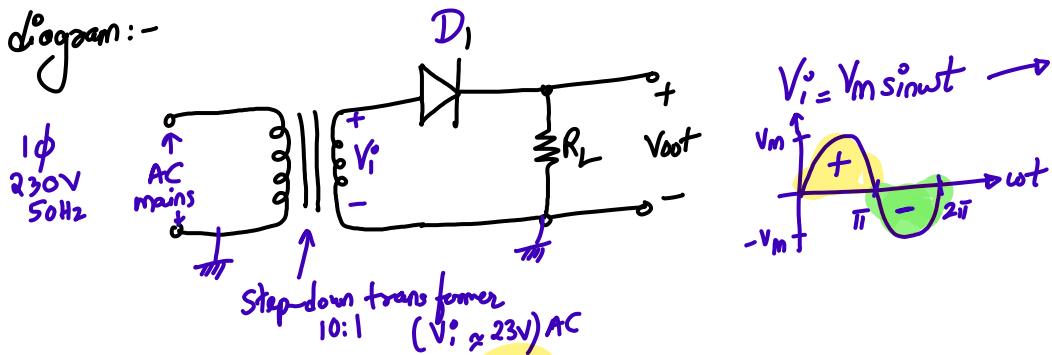

$$V_i = V_m \sin wt \rightarrow \text{Secondary voltage of transformer}$$

Case ①:- During +ve half cycle of $\frac{1}{2}p(V_i)$

D_1 is F.B i.e ON

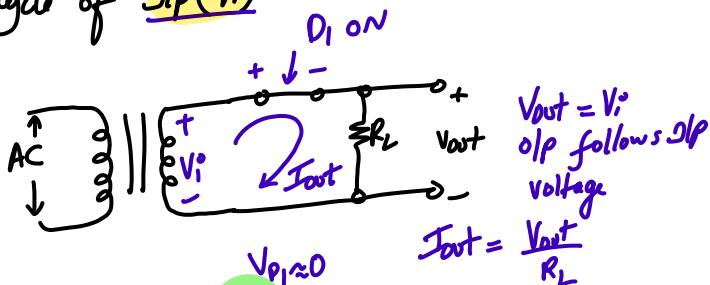


$$V_{out} = V_i \\ \text{o/p follows o/p voltage}$$

$$I_{out} = \frac{V_o}{R_L}$$


Case ②:- During -ve half cycle of $\frac{1}{2}p(V_i)$

D_1 is R.B i.e OFF

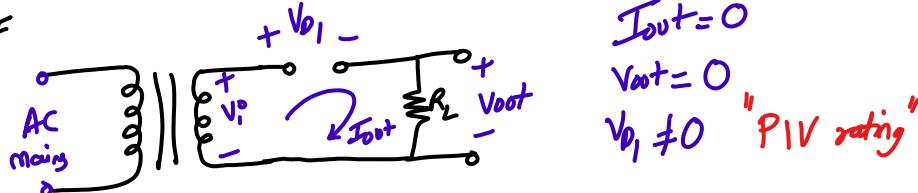

Input-Output wlf's :-
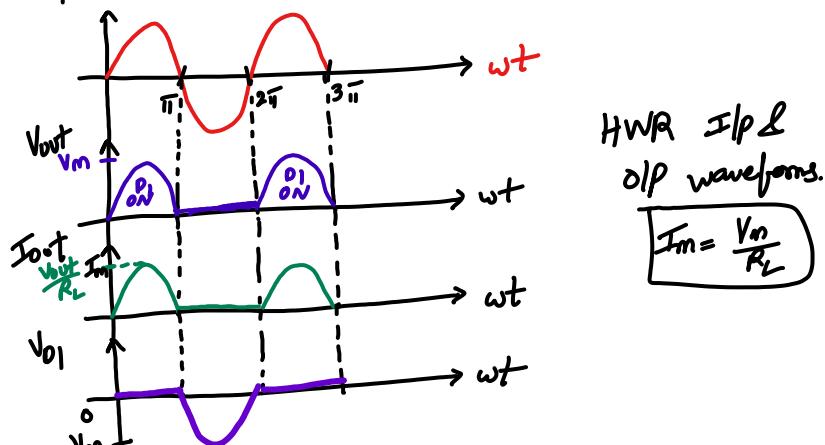
$$\boxed{\begin{aligned} V_{out} &= V_i (\text{if } 0 < wt < \pi) \\ &= 0 \quad \text{if } \pi < wt < 2\pi \end{aligned}} \quad (1)$$



$$\boxed{I_m = \frac{V_m}{R_L}}$$

Analysis (HWR):

- Derive a) Expression for $V_{out \text{ avg}}$
 b) π for $V_{out \text{ rms}}$
 c) π for rectification efficiency (η)
 d) π for ripple factor (r)
 e) π for TUF

a) $V_{out(\text{avg})} / V_{dc}$:

$$V_{out(\text{avg})} = \frac{1}{T} \int_0^T V_{out} dt$$


$$V_{out(\text{avg})} = \frac{1}{2\pi} \int_0^{2\pi} V_{out} dt$$

$$V_{out(\text{avg})} = \frac{1}{2\pi} \left[\int_0^{\pi} V_m \sin \omega t dt + \int_{\pi}^{2\pi} 0 dt \right]$$

$$V_{out(\text{avg})} = \frac{V_m}{2\pi} \left[-\cos \omega t \right]_0^{\pi} = -\frac{V_m}{2\pi} [\cos \pi - \cos 0]$$

$$V_{out(\text{avg})} = \frac{V_m}{2\pi} (2)$$

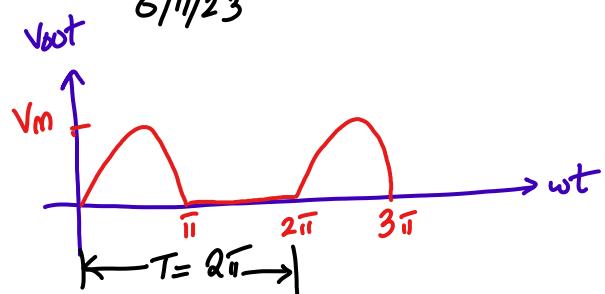
$$V_{out(\text{avg})} = \frac{V_m}{\pi} \quad \text{i.e. } V_{dc} = 0.318 V_m$$



$$V_i = V_m \sin \omega t$$

 $\frac{2\pi}{\pi}$

$$\int_0^{\pi} 0 dt$$

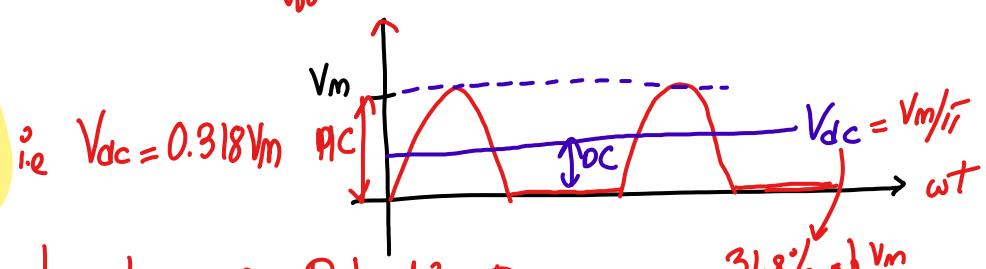 $\frac{V_m}{2\pi}$ V_{out} 

o/p of HWR: Pulsating DC
(AC+DC)

$$I_{out(\text{avg})} = I_{dc} = \frac{V_{out(\text{avg})}}{R_L} = \frac{V_{dc}}{R_L} = \frac{V_m}{\pi R_L} I_m$$

$$I_{out(\text{avg})} = \frac{I_m}{\pi} \quad \text{where } I_m = \frac{V_m}{R_L}$$

b) $V_{out(\text{rms})} \rightarrow$ RMS value of AC component of o/p

$$V_{out}^2(\text{rms}) = \frac{1}{T} \int_0^T V_{out}^2(wt) dt \quad ; \quad T = 2\pi$$

$$V_i = V_m \sin \omega t$$

$$V_{out}^2(\text{rms}) = \frac{1}{2\pi} \int_0^{2\pi} V_{out}^2(wt) dt$$

$$V_{out}^2(\text{rms}) = \frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega t dt = \frac{V_m^2}{2\pi} \int_0^{\pi} \left(1 - \frac{\cos 2\omega t}{2}\right) dt$$

$$V_{out}^2(\text{rms}) = \frac{V_m^2}{2\pi} \left\{ \frac{\omega t}{2} - \frac{\sin 2\omega t}{4} \right\}_{wt=0}^{\pi}$$

$$V_{\text{out}}^2(\text{rms}) = \frac{V_m^2}{2\pi} \left\{ \left(\frac{\pi}{2} - \alpha \right) - \frac{\sin 2\alpha}{4} - \frac{\sin \alpha}{4} \right\}$$

$$V_{\text{out}}^2(\text{rms}) = \frac{V_m^2}{2\pi} \times \frac{\pi}{2} = \frac{V_m^2}{4}$$

$$V_{\text{out}}(\text{rms}) = \frac{V_m}{2}$$

$$I_{\text{out}}(\text{rms}) = \frac{I_m}{2}$$

$$I_m = \frac{V_m}{R_L}$$

c) Rectifier efficiency (η): → It is the ratio of DC power at the o/p to the applied AC power

$$\% \eta = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100$$

$$P_{\text{DC}} = V_{\text{dc}} I_{\text{dc}} = \frac{V_{\text{dc}}^2}{R_L} = I_{\text{dc}}^2 R_L$$

$$P_{\text{AC}} = V_{\text{out}}(\text{rms}) I_{\text{out}}(\text{rms}) = V_{\text{rms}} I_{\text{rms}} = \frac{V_{\text{rms}}^2}{R_L} = I_{\text{rms}}^2 R_L$$

$$P_{\text{DC}} = \frac{V_{\text{dc}}^2}{R_L} = \frac{\left(\frac{V_m}{2}\right)^2}{R_L} = \frac{V_m^2}{\pi^2 R_L} \quad \text{--- (a)}$$

$$P_{\text{AC}} = \frac{V_{\text{rms}}^2}{R_L} = \frac{\left(\frac{V_m}{2}\right)^2}{R_L} = \frac{V_m^2}{4 R_L} \quad \text{--- (b)}$$

$$\% \eta = \frac{P_{\text{DC}}}{P_{\text{AC}}} \times 100 = \frac{\frac{V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{4 R_L}} \times 100$$

$$\% \eta = \frac{4}{\pi^2} \times 100$$

$$\% \eta = 40.56 \% \quad \text{HWR}$$

d) Ripple factor (x):

It is the ratio of rms value of o/p AC component to the DC component of rectifier o/p

$$\gamma = \frac{I_{ac}}{I_{dc}}$$

$$I_{ac} = \sqrt{I_{out(m)s}^2 - I_{dc}^2}$$

i.e. $\frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{ms}^2}{I_{dc}^2} - 1}$

i.e.
$$\gamma = \sqrt{\frac{I_{ms}^2}{I_{dc}^2} - 1}$$


For HWR, $I_{ms} = \frac{I_m}{2}$, $I_{dc} = \frac{I_m}{\pi}$

$$\gamma = \sqrt{\frac{\frac{I_m^2}{4}}{\frac{\pi^2}{4}} - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$


$\gamma = 1.21$ _{HWR}

— X —

Full-wave rectifier with 'R' load:

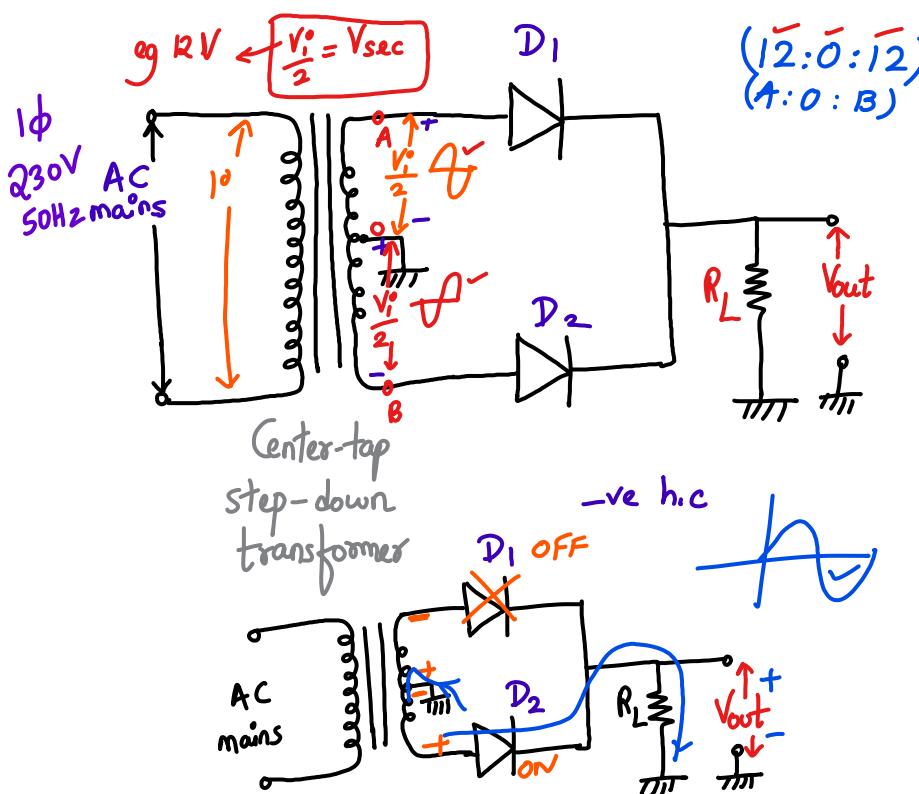

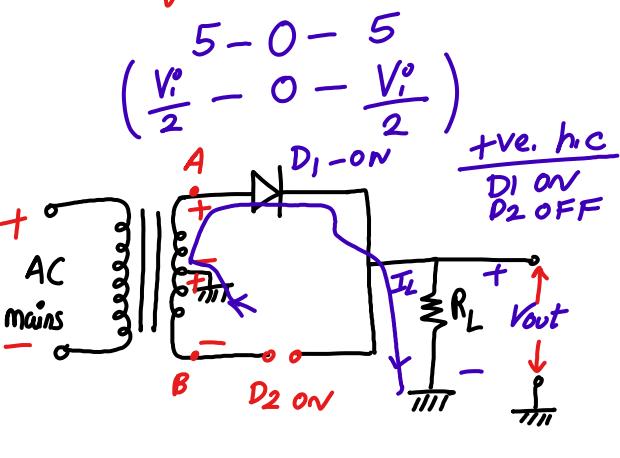
$V_i^o \Rightarrow$ Secondary voltage of transformer




$$V_{out} = \frac{V_i^o}{2} (\sqrt{m} \sin \omega t) \text{ if } 0 < \omega t < \pi$$

$$= \frac{V_i^o}{2} (\sqrt{m} \sin \omega t) \text{ if } \pi < \omega t < 2\pi$$


①

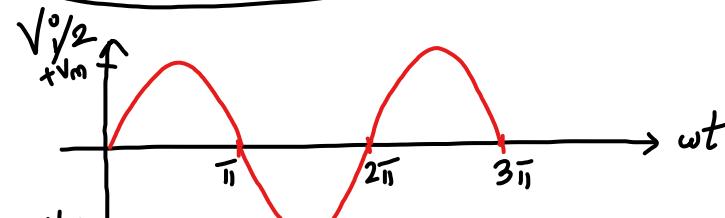

$$V_{out} = I_{out} R_L$$

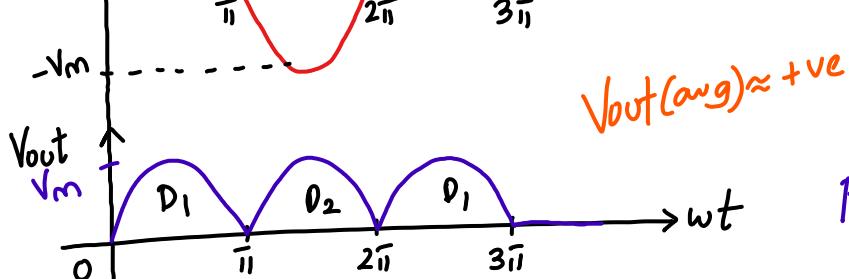

FWR I/P &
O/P waveforms

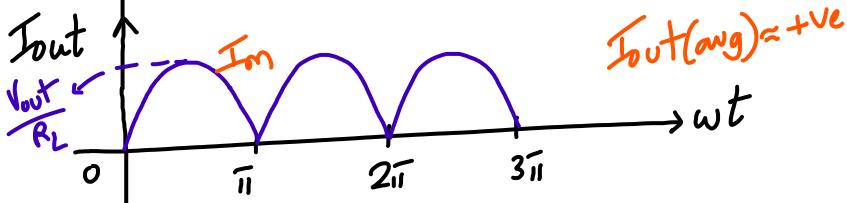

$$I_{out(\text{avg})} \approx +ve$$

$$Im = \frac{V_m}{R_L}$$

FWR with 'R' load analysis:

- { Derive a) Expression for rectification efficiency (η) }
- b) Expression for ripple factor (γ) }
- c) Expression for TUF }

$$\textcircled{1} \quad V_{\text{out(avg)}} = V_{\text{dc}} = \frac{1}{T} \int_0^T V_{\text{out}} dt$$

i.e. $V_{\text{dc}} = \frac{1}{\pi} \int_0^{\pi} v_i(\omega t) dt$

i.e. $V_{\text{dc}} = \frac{1}{\pi} \left[\int_0^{\pi} V_m \sin \omega t dt \right]$

i.e. $V_{\text{dc}} = \frac{V_m}{\pi} [-\cos \omega t]_{\omega t=0}$



i.e. $V_{\text{dc}} = \frac{V_m \times \{-[\cos \pi - \cos 0]\}}{\pi} = \frac{V_m}{\pi} \times -1 \times (-2)$

i.e. $V_{\text{dc}} = \frac{2V_m}{\pi}$

FWR

$V_{\text{out(avg)}}$

i.e. $V_{\text{dc}} = 0.636 V_m$

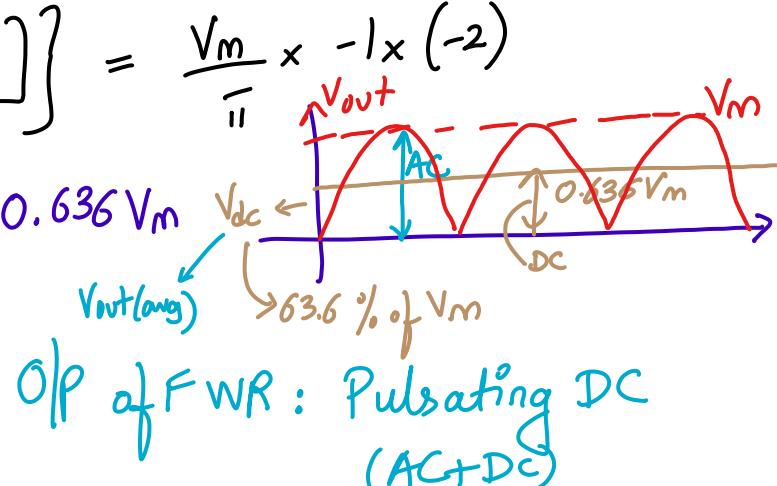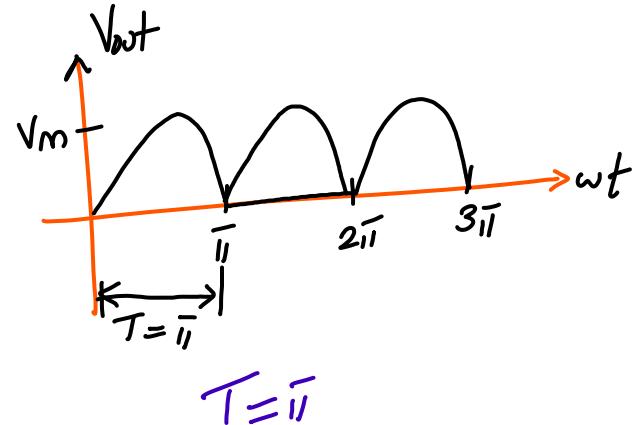

$$V_{\text{out(avg)}} = V_{\text{dc}} = \frac{2V_m}{\pi}$$

$$\textcircled{2} \quad I_{\text{out(avg)}} = \frac{V_{\text{out(avg)}}}{R_L} = \frac{V_{\text{dc}}}{R_L} = \frac{2V_m}{\pi R_L} \xrightarrow{\text{Im}} \left(V_{\text{out(avg)}} = I_{\text{out(avg)}} R_L \right)$$

$$I_{\text{out(avg)}} = \frac{2 \text{Im}}{\pi}$$

where, $\boxed{\text{Im} = V_m/R_L}$

$$I_{\text{out(avg)}} = I_{\text{dc}}$$

\textcircled{3} $V_{\text{out(rms)}}$ \rightarrow RMS value of AC component of output

$$V_{\text{out(rms)}} = \left[\frac{1}{T} \int_0^T V_{\text{out}}^2(wt) dwt \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{1}{\pi} \int_0^{\pi} V_i^2(wt) dwt \right]^{1/2}$$

$$\bar{T} = \pi$$

For m eq^n \textcircled{1},

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{1}{\pi} \left\{ \int_0^{\pi} V_m^2 \sin^2 wt dwt \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{V_m^2}{\pi} \left\{ \int_0^{\pi} \left(1 - \frac{\cos 2wt}{2} \right) dwt \right\} \right]^{1/2}$$

$$\sin^2 x = \frac{1 - \cos 2x}{2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{V_m^2}{2\pi} \left\{ \left. wt - \frac{\sin 2wt}{2} \right|_{wt=0}^{\pi} \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{V_m^2}{2\pi} \left\{ (\pi - 0) - \frac{\sin 2\pi}{2} - \frac{\sin 0}{2} \right\} \right]^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \left[\frac{V_m^2}{2\pi} \times \pi \right]^{1/2} = \left(\frac{V_m^2}{2} \right)^{1/2}$$

$$\text{i.e } V_{\text{out(rms)}} = \frac{V_m}{\sqrt{2}}$$

FWR

where,

$$I_{\text{out rms}} = \frac{\text{Im}}{\sqrt{2}}$$

$$\boxed{\text{Im} = \frac{V_m}{R_L}}$$

$$V_{\text{out(rms)}} = V_{\text{rms}} ; I_{\text{out rms}} = I_{\text{rms}}$$

④ Rectification efficiency (η):

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100$$

It is the ratio of DC power at the output to the applied input AC power

$$P_{DC} = V_{dc} I_{dc} = \frac{V_{dc}^2}{R_L} = \overline{I_{dc}^2} R_L$$

$$P_{AC} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R_L} = \overline{I_{rms}^2} R_L$$

$$\text{ie } P_{DC} = \frac{V_{dc}^2}{R_L} = \frac{\left(\frac{2V_m}{\pi}\right)^2}{R_L} = \frac{4V_m^2}{\pi^2 R_L} \quad - (a)$$

$$\text{ie } P_{AC} = \frac{V_{rms}^2}{R_L} = \frac{\left(\frac{V_m}{\sqrt{2}}\right)^2}{R_L} = \frac{V_m^2}{2 R_L} \quad - (b)$$

$$\text{ie } \% \eta = \frac{P_{DC}}{P_{AC}} \times 100 = \frac{\frac{4V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{2 R_L}} \times 100 = \frac{8}{\pi^2} \times 100$$

$$\text{i.e. } \% \eta = \frac{8}{\pi^2} \times 100 \approx 81.05\%$$

Rectification efficiency of FWR with R' load

* $\eta_{FWR} > \eta_{HWR}$

⑤ Ripple factor (γ):

It is the ratio of rms value of AC component to the DC component of the rectifier output

Smaller the AC component \rightarrow more effective is the rectifier

$$\gamma = \frac{I_{ac}}{I_{dc}} = \frac{V_{ac}}{V_{dc}}$$

$$; I_{ac} = \sqrt{I_{out(rms)}^2 - I_{dc}^2}$$

Remember it!

$$ie \frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$ie \gamma = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$I_{out(rms)}^2 = I_{rms}^2$$

$$For FWR, I_{rms} = \frac{Im}{\sqrt{2}}, I_{dc} = \frac{Im \times 2}{\pi}$$

$$\gamma = \sqrt{\frac{\frac{Im^2}{2}}{\frac{4 \cdot \frac{Im^2}{\pi^2}}{\pi^2}} - 1} = \sqrt{\frac{\pi^2}{4} - 1}$$


$$\gamma = \sqrt{\frac{\pi^2}{8} - 1} \approx 0.483$$

Fwctr

$$\gamma_{FWR} < \gamma_{HWR}$$



\hookrightarrow contains smaller ac component

Full-wave Bridge rectifier


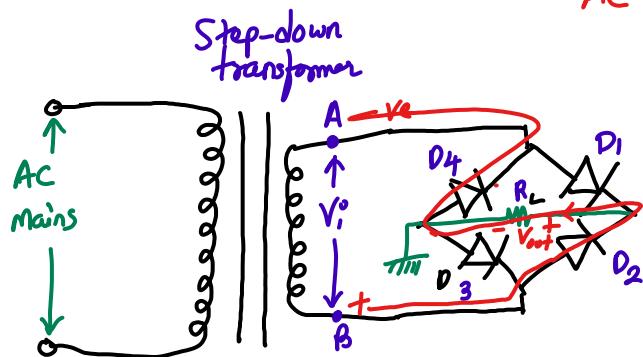


+ve h.c. of $V_i^o \rightarrow D_1 \& D_3 \rightarrow ON$
 $I_{out} \rightarrow A - D_1 - R_L - D_3 - B - A$

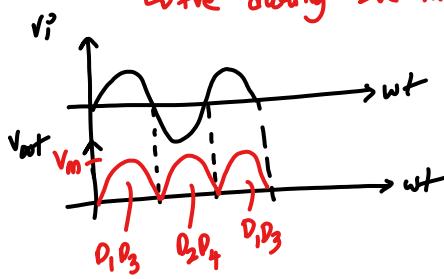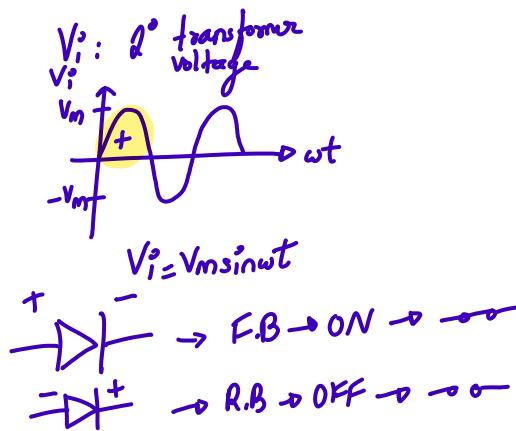-ve h.c. of $V_i^o \rightarrow D_2 \& D_4 \rightarrow ON$
 $I_{out} \rightarrow B - D_2 - R_L - D_4 - A$
 +ve during -ve h.c. also




Full-wave bridge rectifier:

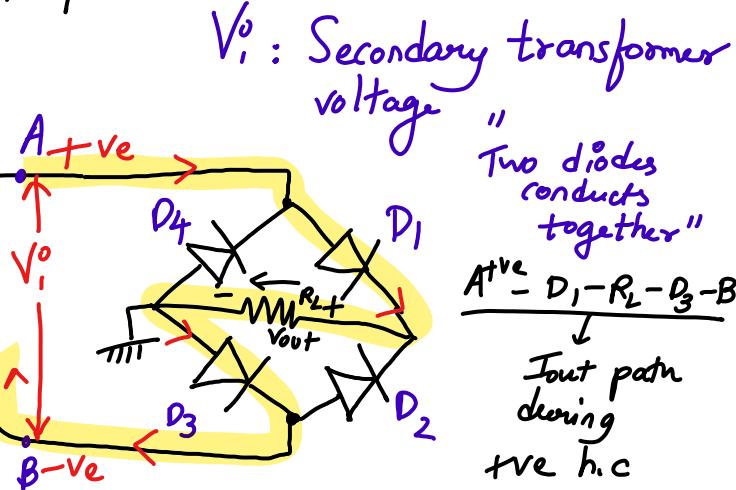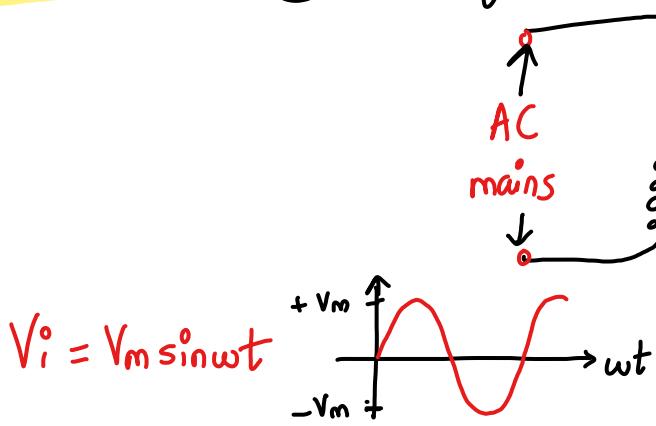

$D_1 \& D_3$: ON (F.B)
 D_2, D_4 : OFF (R.B)



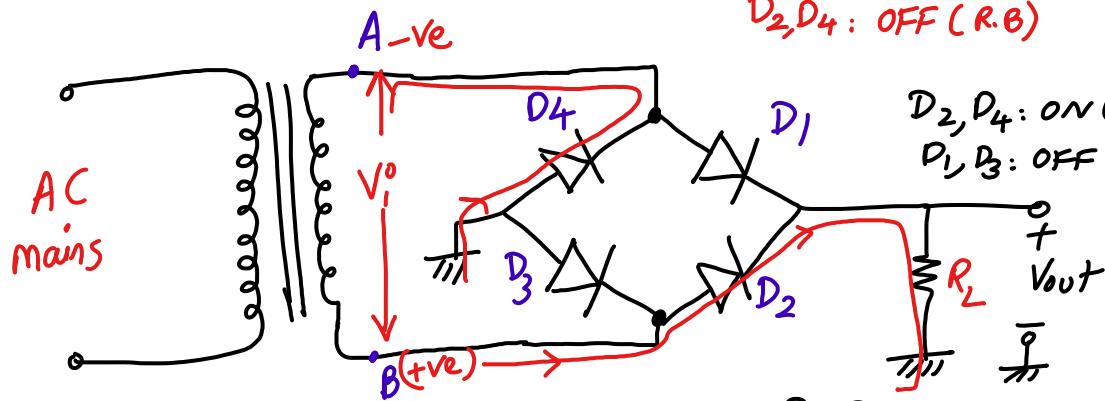
D_2, D_4 : ON (F.B)
 D_1, D_3 : OFF (R.B)



$$V_{out} = V_i^o (\sqrt{m} \sin \omega t) \quad \text{if } 0 \leq \omega t \leq \pi$$

$$= V_i^o (\sqrt{m} \sin \omega t) \quad \text{if } \pi \leq \omega t \leq 2\pi$$

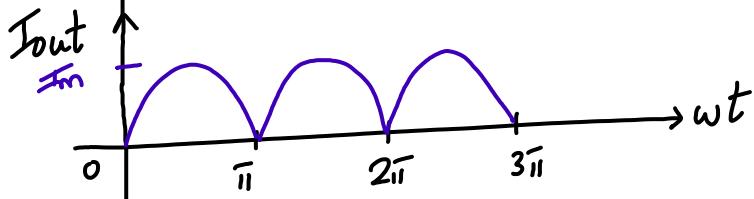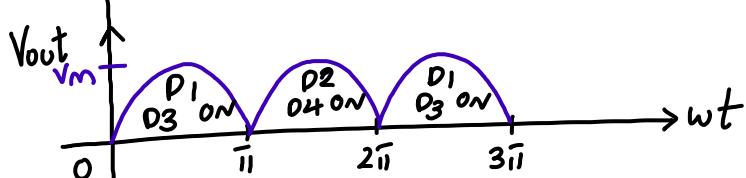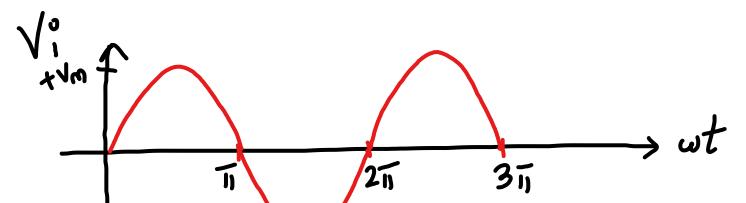$B - D_2 - R_L - D_4 - A$
Iout path during -ve h.c



FWBR I/P - O/P
waveform's

Due to 'R' load, nature of Vout & Iout are similar

'B' with 'R' load analysis:

Derive a) Expression for rectification efficiency (η)

b) Expression for ripple factor (γ)

c) Expression for TUF

$$\textcircled{1} \quad V_{\text{out(avg)}} = V_{\text{dc}} = \frac{1}{T} \int_0^T V_{\text{out}} \, dt$$

$$V_{\text{out(avg)}} = V_{\text{dc}} = \frac{2V_m}{\pi}$$

$$I_{\text{dc}} = \frac{2I_m}{\pi}$$

$$\textcircled{2} \quad I_{\text{out(avg)}} = \frac{V_{\text{out(avg)}}}{R_L} \quad (V_{\text{out(avg)}} = I_{\text{out(avg)}} R_L)$$

\textcircled{3} \quad V_{\text{out(rms)}} \rightarrow \text{RMS value of AC component of output}

$$V_{\text{out(rms)}} = \left[\frac{1}{T} \int_0^T V_{\text{out}}^2(wt) dwt \right]^{1/2}$$

$$\boxed{V_{\text{out(rms)}} = V_{\text{rms}} = \frac{V_m}{\sqrt{2}}} \quad \hookrightarrow \text{FWBR}$$

$$\boxed{I_{\text{rms}} = \frac{I_m}{\sqrt{2}}}$$

④ Rectification efficiency (η):

$$\% \eta = \frac{P_{DC}}{P_{AC}} \times 100$$

It is the ratio of DC power at the output to the applied input AC power

$$P_{DC} = \frac{V_{dc}^2}{R_L}$$

$$\% \eta = \frac{\frac{4V_m^2}{\pi R_L}}{\frac{V_m^2}{2R_L}} \times 100$$

$$P_{AC} = \frac{V_{rms}^2}{R_L}$$

$$\boxed{\% \eta = \frac{8}{\pi^2} \times 100 = 81.05\%}$$

FWBR

⑤ Ripple factor (γ):

It is the ratio of rms value of AC component to the DC component of the rectifier output

Smaller the AC component \rightarrow more effective is the rectifier

$$\gamma = \frac{I_{ac}}{I_{dc}}$$

$$; I_{ac} = \sqrt{I_{out(rms)}^2 - I_{dc}^2}$$

$$\text{i.e. } \frac{I_{ac}}{I_{dc}} = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$\text{i.e. } \boxed{\gamma = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}}$$

for FWBR,

$$\gamma = \sqrt{\frac{\left(\frac{Im}{\sqrt{2}}\right)^2}{\left(\frac{2Im}{\pi}\right)^2} - 1}$$

$$\gamma = \sqrt{\frac{\frac{Im^2\pi^2}{4}}{2 \times 4 Im^2} - 1} = \sqrt{\frac{\pi^2}{8} - 1} = 0.483$$

$$\boxed{\gamma = 0.483 \text{ FWBR}}$$